

# APPLICATION NOTE

## **ABSTRACT**

Despite the relatively simple interconnections in the DAA, extraordinary attention should be given to the layout of the DAA since it directly connects to the network. Both Part 15 and Part 68 of FCC regulations should be considered by the engineer during the layout process.

## **AN810**

### **DAA printed circuit board layout**

2000 Jan 27

# DAA printed circuit board layout

# AN810

## INTRODUCTION

Despite the relative simple interconnections in the DAA, extraordinary attention should be given to the layout of the DAA since it directly connects to the network. Both Part 15 and Part 68 of FCC regulations should be considered by the engineer during the layout process.

## EMI SUPPRESSION (Part 15b)

Most significant sources of EMI are:

- Clock traces
- Fast clock
- Two or more clocks in the same system
- High impedance ground return wires (long traces)
- Inadequate or improper power supply de-coupling
- I/O connectors where cables exist or enter the system

In order to achieve low EMI emission it is advisable to keep all clock traces as short as possible and as far from all other traces as possible, especially analog modem traces. In a system where there is more than one clock, try to keep them in separate areas of the circuit, using separate grounds to prevent them "beating together" to give rise to higher frequencies than either clock's fundamental.

As a preventive measure, add a RC circuit (see Figure 1) as close to the clock source as possible to try to slow down the clock edge if necessary. The value for the resistor and capacitor varies depend on the clock source and the slowness for the clock edge. If the RC circuit is not needed, the resistor can be shorted with a zero ohm resistor or jumper wire and the capacitor can be omitted.

 


Figure 1. RC circuit

Don't use a clock source with more drive capability (i.e., fast rise/fall time of the clock edge) than necessary. In this respect it is better to use a crystal as a clock source rather than an oscillator, since oscillators usually provide maximum drive and fastest slew rate, significantly increasing the device's EMI emission.

All ICs should be bypassed with capacitors close to the power supply pins. Additional caps should be placed along the supply traces to ground to prevent long loop current. The supplies to the sensitive analog components such as the analog front end, operational amplifiers in the line interface hybrid must be keep separate from any digital power supplies. These supplies should be bypassed with a high quality tantalum capacitor with a value about 22  $\mu$ F or larger, and a low inductance ceramic capacitor of value of 0.1  $\mu$ F. The 22  $\mu$ F cap is used to decouple the low frequency while the 0.1  $\mu$ F is used to decouple the high frequency. One of the most common mistakes of placing bypass capacitors for a surface mount

device IC on a multiple layers board, is to have the bypassing capacitors close to the power supply pads without actually having short traces from the pads to the capacitors (see Figures 2 and 3).

 


Figure 2. Incorrect way of placing bypass capacitor

 


Figure 3. Correct way of placing bypass capacitor

The speaker ground and amplifier's power connections are quite capable of influencing the performance of the modem; since they involve amplification of the input signal by as much as 20 to 30 dB, and dumping that current into the system ground at the speaker. The effect is very noticeable if the speaker is on during the modem handshake stage, causing the modem to connect at lower speed or occasion retrain if the speaker is also on after the modem has made a connection to the remote modem.

Keep the speaker circuit away from the DAA and the modem transmit and receive circuits. Use a separate power supply for the speaker amplifier and route the speaker's ground back to the system digital ground instead of the system analog ground.

Most often failure of FCC Part 15 can be traced back to the cables that connect the system to the outside world — phone lines, speaker cable and microphone cable. High frequency signals can be blocked before they get out onto the cables by placing inductors in series with the cables at the exit points. One type of such inductor commonly used are ferrite-beads. Depending on the type, the impedance at the frequency of interest varies from 100  $\Omega$  to greater than a 1000  $\Omega$ . Use beads with impedance of about 400–500  $\Omega$  over the frequency of interest (1 MHz – 500 MHz). You can use beads with higher impedance but they will cost a lot more.

Capacitors are also used to bypass high frequency signals to earth. They are often connected to the tip and ring of the RJ-11 jack and to earth ground. The most typical values in modem applications you often see are 470 pF – 1000 pF, however, the capacitors are in the DAA side of the system, they must have a rating of at least 1500 V, although 2000 V rating are often used.

# DAA printed circuit board layout

# AN810

## TELEPHONE NETWORK INTERFACE (Part 68): Hazardous Voltage and DAA Layout

A high voltage, 1500 V, is placed between the tip and ring of the RJ-11 jack and the system ground to simulate a lightning strike. If a low impedance path exists between the DAA and the rest of the system, some traces may be burned, or some components may catch fire. To protect against this test, there must be a barrier between the DAA and the rest of the system.

The network side contains the line and phone jacks, current limiting resistors, ferrite beads, the ring detector circuit, surge protector, etc. The transformer, the ring detector optoisolator, and the hook-relay are crossed between the network side and the system side. Therefore these components must be chosen to withstand high

voltages, up to 1500 VAC. A surge protector (MOV) or a spark gap is also used for extra protection, and they must be placed close to the RJ-11 with heavy traces. These devices should not conduct below the ringing voltage, and sometimes in rare cases the ringing voltage can be as much as 310 VAC. To limit the energy dissipated in this device, two current limiting resistors are added in series with tip and ring, and a total of about 20  $\Omega$  is typical.

There should be no traces that cross the barrier, either entering it or passing through it to go somewhere else (see Figure 4). Remove all ground planes and  $V_{CC}$  planes within the Network Side. Use heavy traces of at least 12 mil for all traces in the Network Side. Try to put as much space between these traces as possible. Avoid a zig-zag pattern, or 90 degree angle routing.

 


Figure 4. DAA board layout

SC00201

# DAA printed circuit board layout

# AN810

## POWER SUPPLY AND GROUNDING FOR UCB1200/1300

When using a single power supply, as suggested in the reference schematic shown in Figure 5,  $V_{CCA1}$  and  $V_{CCA2}$  should be derived from the cleanest power supplies available.

The UCB1200/1300 and its analog circuitries should be placed close together, and should have its own ground plane. The UCB1200/1300 analog and digital ground pins should be connected to this ground plane which in turn should be connected to the rest of the system ground by a ferrite bead.

Although not shown in the figures, traces bringing power to the UCB1200/1300 ( $V_{CCA1}$ ,  $V_{CCA2}$ ,  $V_{DD1}$ ,  $V_{DD2}$ ) should be as wide as possible, at least 50 mil, to keep the impedance low. Likewise for power and ground vias, they should be as large as possible.

Here is a list of guidelines for optimum printed circuit board layout.

1. Group the analog components together in one area and the digital components in a separate area.
2. Split the ground plane into separate digital and analog ground planes with digital components placed above the digital ground plane, and analog components above the analog ground plane as shown on Figure 6. The digital pins and analog pins should be connected to their own plane with very low impedance vias.
3. The ground plane split should be underneath the digital section of the chip.
4. The digital and analog ground planes should be connected together at one point and that point should be near the power supply.
5. Analog trace should be routed over the analog plane and the digital traces should be routed over the digital plane.
6. Keep digital traces and clock away from the analog area.
7. Decoupling capacitors should be placed as close to the IC as possible. (Refer to Figure 7.)
8. Use additional bypass capacitors along all power and ground traces to provide short, low impedance loops for ground currents pulses generated by high-frequency switching.
9. Power supply terminals should be shunted by quality tantalum capacitors in the order of 10  $\mu\text{F}$ .
10. To reduce EMI emission from digital signal and clock, do not route the traces with 90 degree bend, use two 45 degree turn instead.
11. Use very short traces for clocks.
12. Keep the audio amplifier and speaker ground away from the rest of the modem portion due to:
  - a. the magnitude of the audio current pumped into the ground (a few hundred mW peak).
  - b. audio signals are amplified during the initial handshake.
  - c. audio spectrum falls over the receive signal.


 


Figure 5. Power supply and grounding circuit

# DAA printed circuit board layout

# AN810

 

SC00197

Figure 6. UCB1300 recommended ground plane

# DAA printed circuit board layout

# AN810

 


Figure 7. Printed circuit board layout for UCB1300

---

# DAA printed circuit board layout

AN810

---

## INTRODUCTION

---

# DAA printed circuit board layout

AN810

---

## Definitions

**Short-form specification** — The data in a short-form specification is extracted from a full data sheet with the same type number and title. For detailed information see the relevant data sheet or data handbook.

**Limiting values definition** — Limiting values given are in accordance with the Absolute Maximum Rating System (IEC 134). Stress above one or more of the limiting values may cause permanent damage to the device. These are stress ratings only and operation of the device at these or at any other conditions above those given in the Characteristics sections of the specification is not implied. Exposure to limiting values for extended periods may affect device reliability.

**Application information** — Applications that are described herein for any of these products are for illustrative purposes only. Philips Semiconductors make no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

## Disclaimers

**Life support** — These products are not designed for use in life support appliances, devices or systems where malfunction of these products can reasonably be expected to result in personal injury. Philips Semiconductors customers using or selling these products for use in such applications do so at their own risk and agree to fully indemnify Philips Semiconductors for any damages resulting from such application.

**Right to make changes** — Philips Semiconductors reserves the right to make changes, without notice, in the products, including circuits, standard cells, and/or software, described or contained herein in order to improve design and/or performance. Philips Semiconductors assumes no responsibility or liability for the use of any of these products, conveys no license or title under any patent, copyright, or mask work right to these products, and makes no representations or warranties that these products are free from patent, copyright, or mask work right infringement, unless otherwise specified.

---

Philips Semiconductors  
811 East Arques Avenue  
P.O. Box 3409  
Sunnyvale, California 94088-3409  
Telephone 800-234-7381

© Copyright Philips Electronics North America Corporation 2000  
All rights reserved. Printed in U.S.A.

Date of release: 02-00

Document order number:

9397 750 06844

*Let's make things better.*