

Transmit Gain Adjustments For The MC34014 Speech Network

By
Scott Bader and Dennis Morgan
Bipolar Analog IC Division

INTRODUCTION

The MC34014 telephone speech network provides for direct connection to an electret microphone and to Tip and Ring. In between, the circuit provides gain, drive capability, and determination of the ac impedance for compatibility with the telephone lines. Since different microphones have different sensitivity levels, different gain levels are required from the microphone to the Tip and Ring lines. This application note will discuss how to change the gain level to suit a particular microphone while not affecting the other circuit parameters.

CIRCUIT DESCRIPTION

Refer to Figure 1. The microphone is assumed to be an electret type, characterized by a high dynamic impedance. It is therefore considered to be an ac current source rather than a voltage source. If the microphone used has a dynamic impedance which is not high (compared to R_g), then the microphone must be modeled as a current source paralleled by its dynamic impedance. That impedance value must then be considered to be in parallel with R_g in the following equations. The T_x amplifier has a fixed gain of -20 , and the EQ amplifier gain varies from 0.25 to 0.75, depending on the loop current. Z_L is the line impedance. The transmit gain is defined as V_+/I_{mic} and is equal to:

$$\frac{V_+}{I_{mic}} = \frac{R_g \times Z_L \times A_{TX}}{(1 + R_g/R_A)R_g + (A_{TX})(A_{EQ})(Z_L)}$$

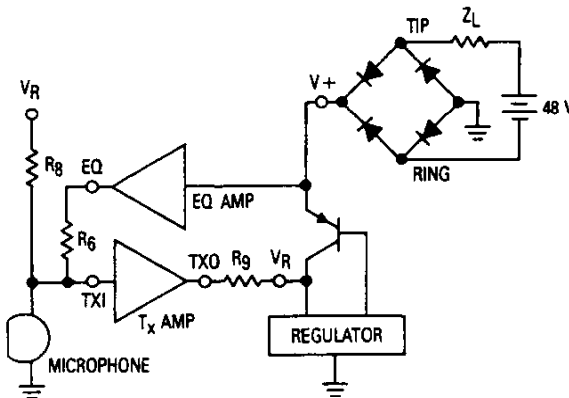


Figure 1. MC34014 Transmit Section

where A_{TX} = gain of the transmit amplifier (20 V/V)
 A_{EQ} = gain of the equalization amp. (0.25 to 0.75 V/V)
 R_A = $R_g/10 \text{ k}\Omega$ ($10 \text{ k}\Omega$ = input impedance of Tx amp.)

The ac impedance of the circuit is defined as:

$$Z_{ac} = \frac{R_g (1 + R_g/R_A)}{(A_{TX})(A_{EQ})}$$

The receive gain (see data sheet for the equivalent circuit) is defined as:

$$G_{rx} = \frac{R_4}{R_1} + \frac{(X_C/R_2)(A_{EQ})(A_{TXO})(A_{STA}) \times R_4}{((X_C/R_2) + R_3)(1 + R_g/R_A) \times R_2}$$

As can be seen from the above equations, changing R_g while maintaining the R_g/R_A ratio constant will result in a transmit gain change (proportional to R_g) but will not affect the other parameters. For example, increasing R_g and R_6 by a factor of 3 will increase the transmit gain by $\approx 10 \text{ dB}$.

Using the above procedure to increase the transmit gain results in increasing R_g , which supplies the bias current to the microphone. If the higher value of R_g results in insufficient bias voltage at the microphone, then the alternate biasing scheme of Figure 2 should be used.

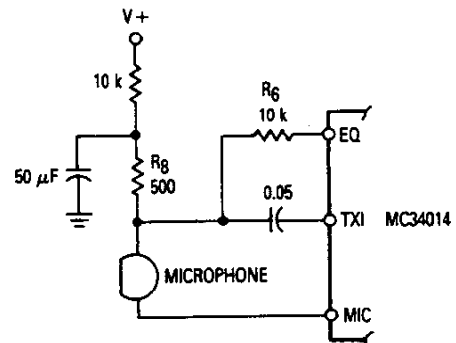


Figure 2. Alternate Biasing Scheme for Higher Voltage Microphones




TEST RESULTS

Tests were conducted with a Primo EM-95A microphone, having a sensitivity of $-53 \text{ dB} \pm 3 \text{ dB}$ ($0 \text{ dB} = 1 \text{ V}/\mu\text{bar}$), and a Hosiden KUC2123 microphone which has a sensitivity of $-60 \text{ dB} \pm 3 \text{ dB}$. The test circuit is shown in Figure 3. The tests consisted of applying a constant sound level to the microphones, and measuring the output at V_{CO} , while simulating line lengths of 0–21 Kfeet. The outputs of the two circuits were nearly identical at all line lengths.

CONCLUSION


Although the designs of the various parameters (transmit gain, receive gain, ac impedance, etc.) of the MC34014 speech network are not mutually exclusive due to the commonality of various components, it is possible to adjust the transmit gain independently to suit a particular microphone.

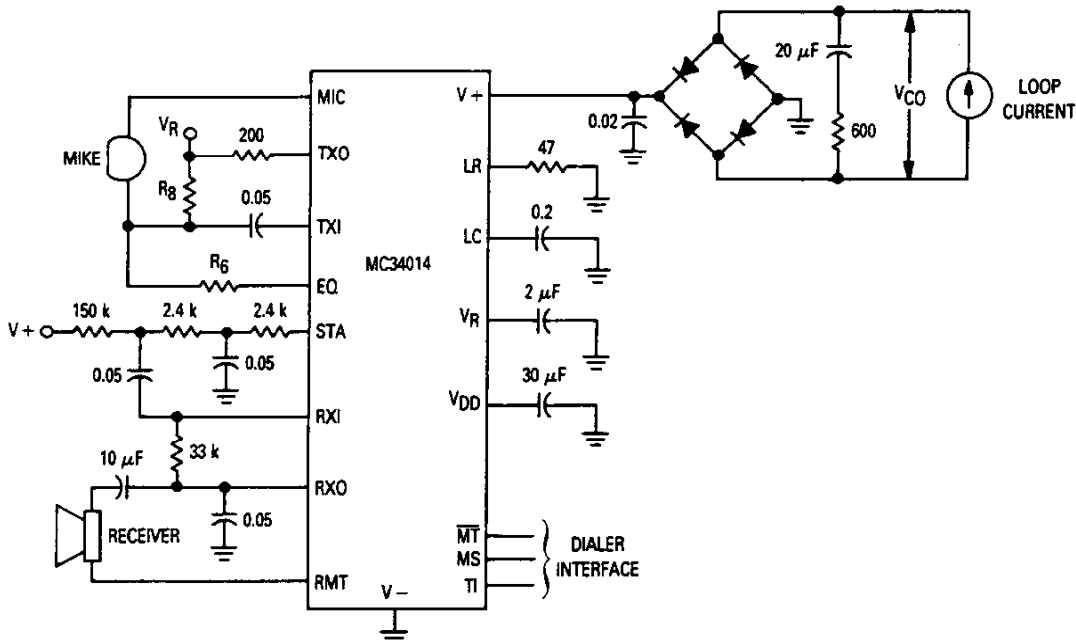For further information on the MC34014 speech network, refer to the data sheet.



For Primo EM-95A microphone $R_8 = 500 \Omega$, $R_6 = 10 \text{ k}$
 For Hosiden KUC2123 microphone $R_8 = 1.5 \text{ k}$, $R_6 = 30 \text{ k}$

Figure 3. Microphone Gain Test Circuit

Motorola reserves the right to make changes without further notice to any products herein. Motorola makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does Motorola assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation consequential or incidental damages. "Typical" parameters can and do vary in different applications. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. Motorola does not convey any license under its patent rights nor the rights of others. Motorola products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the Motorola product could create a situation where personal injury or death may occur. Should Buyer purchase or use Motorola products for any such unintended or unauthorized application, Buyer shall indemnify and hold Motorola and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that Motorola was negligent regarding the design or manufacture of the part. Motorola and  are registered trademarks of Motorola, Inc. Motorola, Inc. is an Equal Opportunity/Affirmative Action Employer.

Literature Distribution Centers:

USA: Motorola Literature Distribution; P.O. Box 20912; Phoenix, Arizona 85036.

EUROPE: Motorola Ltd.; European Literature Centre; 88 Tanners Drive, Blakelands, Milton Keynes, MK14 5BP, England.

JAPAN: Nippon Motorola Ltd.; 4-32-1, Nishi-Gotanda, Shinagawa-ku, Tokyo 141, Japan.

ASIA PACIFIC: Motorola Semiconductors H.K. Ltd.; Silicon Harbour Center, No. 2 Dai King Street, Tai Po Industrial Estate, Tai Po, N.T., Hong Kong.



MOTOROLA
 JIT PRINTED IN USA (1994) MPS/POD

AN958/D

