

APPLICATION NOTE

**Application of the TEA1097
Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs
and analog multiplexer**

AN98077



**TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer**

Application Note

Abstract

The TEA1097 is a bipolar circuit which includes line interface, loudspeaker and microphone amplifiers and switches for connection of auxiliary interfaces. It is intended to be used in line or mains powered telephone terminals.

A detailed description of the circuit blocks of the TEA1097 and advices on adjustments are contained in this report.

APPLICATION NOTE

Application of the TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

AN98077

Authors:

**D. Delbecq, A. Gauthier, J-M. Maurie
Business Line Communication
Caen, France**

Keywords

Telecom
Demonstration Board
TEA1097
transmit
receive
auxiliary
line

Date: July 30th, 1998

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

Summary

A detailed description of the TEA1097 is given.

The TEA1097 incorporates a line interface block with microphone, earphone and DTMF amplifiers.

It incorporates also a base microphone amplifier as well as a loudspeaker amplifier.

In addition, two auxiliary inputs and one auxiliary output combined with integrated switches allow the use of the TEA1097 in a lot of applications which can be either line or mains powered.

A cookbook gives the general application steps.

A demonstration board, OM5848, is available.

Note :

The information **presented** in this document does not form part of any quotation or contract, is believed to be accurate and reliable and may be changed without notice. No liability will be accepted by the publisher for any consequence of its use. Publication thereof does not convey nor imply any licence under patent or other industrial or intellectual property rights.

**TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer**

Application Note**CONTENTS**

1. INTRODUCTION	8
2. BLOCK DIAGRAM	9
3. DESCRIPTION OF THE TEA1097.....	14
3.1 Line interface.....	14
3.1.1 DC characteristics	14
3.1.2 Line impedance	19
3.1.3 Anti-sidetone network	20
3.1.4 Automatic gain control	21
3.2 Supplies	22
3.2.1 Supply VBB	23
3.2.2 Supply VDD.....	26
3.2.3 Microphone supply MICS.....	27
3.3 Transmit.....	27
3.3.1 Handset microphone amplifier	28
3.3.2 DTMF amplifier.....	32
3.3.3 Base microphone amplifier	34
3.3.4 Auxiliary transmit amplifier TXAUX	35
3.4 Receive.....	37
3.4.1 Line receive amplifier RECO.....	38
3.4.2 Earphone amplifier QR	42
3.4.3 Loudspeaker amplifier LSAO	43
3.4.4 Auxiliary receive amplifier AUXO	45
3.4.5 Auxiliary microphone monitor amplifier.....	49
3.5 Logic block.....	52
3.5.1 Logic inputs	52
3.5.2 Connections	53
4. APPLICATION COOKBOOK	56
5. APPLICATION EXAMPLES	59
6. ELECTROMAGNETIC COMPATIBILITY	67
7. REFERENCES	68

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

LIST OF FIGURES

Fig. 1	Block diagram of TEA1097	9
Fig. 2	Pinning of TEA1097	10
Fig. 3	Table of switch management.....	13
Fig. 4	DC characteristics configuration	15
Fig. 5	I _{bb} versus V _{bb}	16
Fig. 6	Main voltages versus line current.....	16
Fig. 7	Low voltage behavior in line powered condition.....	17
Fig. 8	Low voltage behavior when V _{BB} = 5 V	17
Fig. 9	Influence of the R _{va} resistor between REG and SLPE on V _{In} at 15 mA.....	18
Fig. 10	Influence of R _{slpe} on the DC characteristics.....	19
Fig. 11	Equivalent set impedance.....	19
Fig. 12	Anti-sidetone bridge connection.....	20
Fig. 13	Equivalent average line impedance.....	21
Fig. 14	AGC on the microphone gain versus line current and R _{agc}	22
Fig. 15	Block diagram of the supply block.....	23
Fig. 16	Loudspeaker output power versus input voltage at ESI.....	24
Fig. 17	Current consumption on V _{BB} in "ring mode" versus V _{BB}	26
Fig. 18	Current consumption on V _{DD} at V _{BB} = 0	27
Fig. 19	Block diagram of the transmit part	28
Fig. 20	Handset microphone gain versus frequency: influence of temperature	30
Fig. 21	Distortion on line versus handset microphone signal on TEA1097.....	30
Fig. 22	Distortion of line signal at I _{line} = 4 mA	31
Fig. 23	Handset microphone noise versus line current.....	31
Fig. 24	Common mode rejection ratio on microphone	32
Fig. 25	DTMF gain versus frequency: influence of the temperature	33
Fig. 26	Distortion of the DTMF signal on line versus input signal	33
Fig. 27	Connection of the handsfree electret microphone	34
Fig. 28	Distortion on line versus TXAUX input signal	36
Fig. 29	Transmit noise versus line current	36
Fig. 30	Receive block diagram	37
Fig. 31	Block diagram related to AUXO.....	38
Fig. 32	Receive gain versus frequency: influence of temperature	40
Fig. 33	Distortion on RECO versus input signal on IR.....	40
Fig. 34	Distortion on RECO versus input signal on RAUX.....	41
Fig. 35	Distortion on RECO versus level with 5 k Ω load	41
Fig. 36	Noise on RECO.....	42
Fig. 37	Distortion on QR versus level	43
Fig. 38	Output level in ring mode versus input current at ESI.....	45
Fig. 39	Auxiliary receive gain versus frequency, influence of temperature.....	47
Fig. 40	Distortion on AUXO versus input signal on IR	47
Fig. 41	Distortion on AUXO versus input signal on HFTX	48
Fig. 42	Distortion on AUXO versus level with 5 k Ω load.....	48
Fig. 43	Noise on AUXO with input at IR.....	49
Fig. 44	Noise on AUXO with input at MIC+/MIC-	49
Fig. 45	GND and GNDTX connections	51
Fig. 46	Table of connections	54
Fig. 47	Steps in the design flow of the TEA1097	58

TEA1097 Speech and loudspeaker amplifier IC

Application Note

with auxiliary inputs/outputs and analog multiplexer

Fig. 48 Telephone-Answering Machine + Cordless + Fax connections..... 60
Fig. 49 Group-listenning conversation with antihowling..... 61
Fig. 50 Digital Handsfree application 62
Fig. 51 Answering Machine "on line"..... 63
Fig. 52 Answering Machine: record, listen with base..... 64
Fig. 53 Answering Machine: record or listen with handset..... 65
Fig. 54 Typical external antihowling circuit..... 66
Fig. 55 Schematic of the demoboard..... 72
Fig. 56 component placement diagram of the demoboard..... 73
Fig. 57 Curve ref board of the TEA1097 74

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

1. INTRODUCTION

The TEA1097 is a circuit which offers the normal handset interface, a loudspeaker amplifier and a base microphone amplifier for digital handsfree application, it also incorporates auxiliary amplifiers combined with switches and a logic control block.

It provides a volume control of the loudspeaker amplifier.

A power supply block extracts power from the line in an optimized way for the loudspeaker amplifier; furthermore, this supply block can be powered from any external supply. A stabilized 3.35 V supply is available for peripherals.

This makes the TEA1097 suitable as the core of a combi telecom terminal, such as cordless telephones, telephone-answering machines or fax machines. In combination with the PCD6002, it offers digital handsfree, answering machine, CID/CW and cordless control.

This report gives a detailed description of the TEA1097 and its basic application. The description is given by means of the block diagram of the TEA1097 (§2) and by discussing every detail of the sub-blocks (§3). The application is discussed by giving a guideline for application (the application cookbook §4) and by giving an application example (§5). EMC aspects are also discussed (§6). The appendix contains a list of abbreviations and the demoboard application diagram of the TEA1097.

Note: the values of parameters given in this application note are as accurate as possible, but please, refer to the last product specification for final ones.

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

2. BLOCK DIAGRAM

In this chapter, the block diagram of the TEA1097 is shown by means of fig. 1. The pinning of the TEA1097 is given by means of fig. 2. A short description of the block diagram is given including the function of the external components.

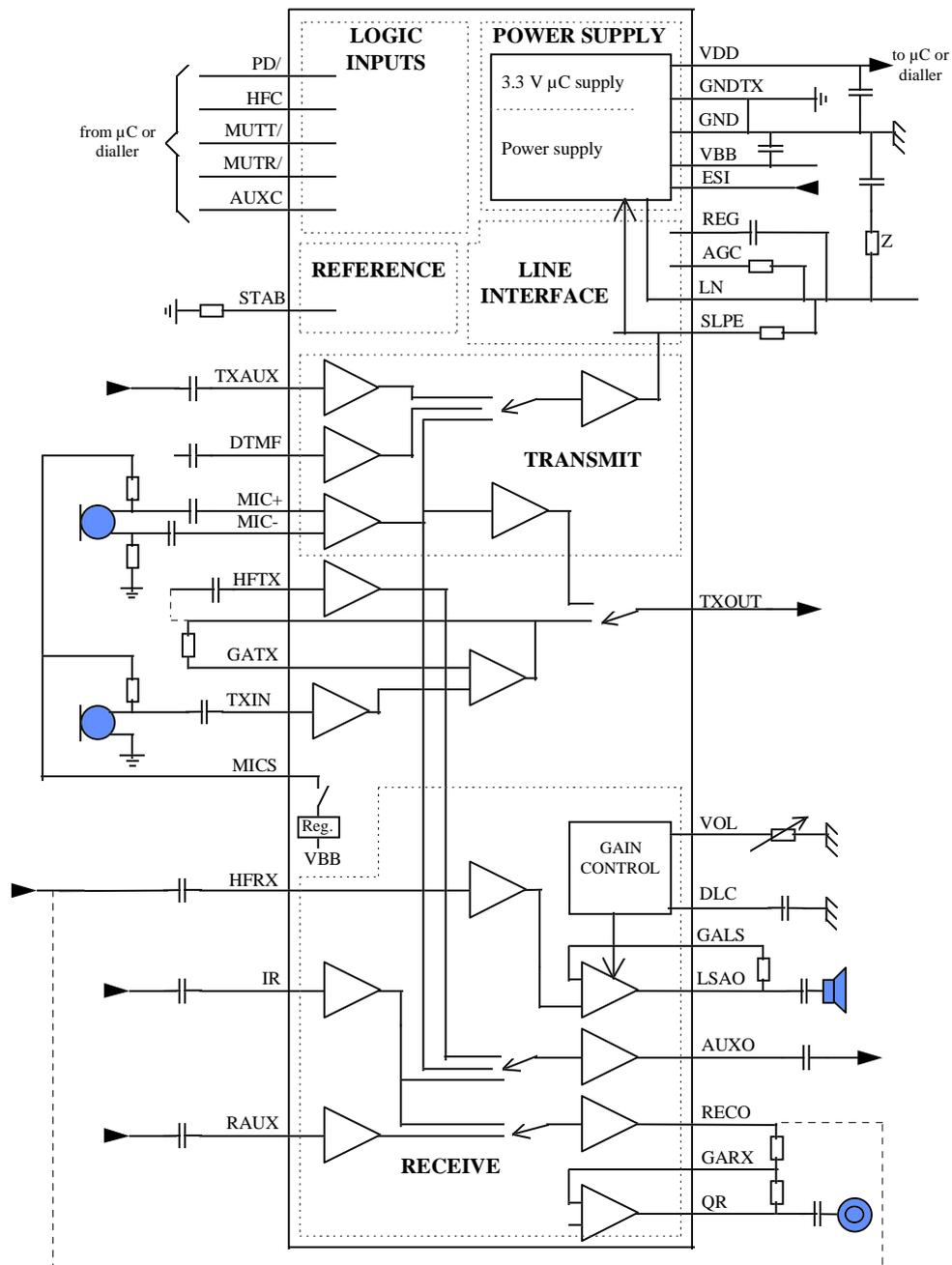


Fig. 1 Block diagram of TEA1097

**TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer**

Application Note

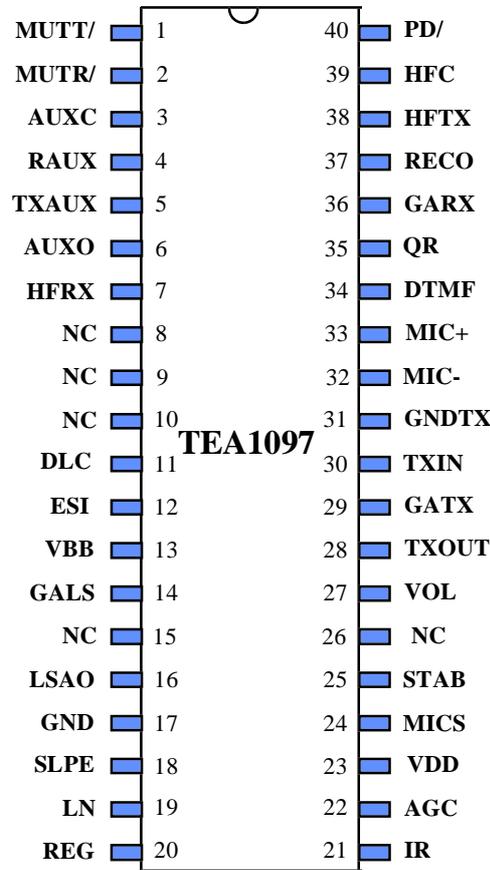


Fig. 2 Pinning of TEA1097

PIN	NAME	DESCRIPTION
1	MUTT/	Logic input
2	MUTR/	Logic input
3	AUXC	Logic input
4	RAUX	Auxiliary receive input
5	TXAUX	Auxiliary transmit input
6	AUXO	Auxiliary output
7	HFRX	Receive input for loudspeaker amplifier
8	NC	no connect
9	NC	no connect
10	NC	no connect
11	DLC	Dynamic limiter
12	ESI	External supply input
13	VBB	Stabilized supply for internal circuitry
14	GALS	Loudspeaker amplifier gain adjustment

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

15	NC	no connect
16	LSAO	Loudspeaker amplifier output
17	GND	Ground reference
18	SLPE	Line current sense
19	LN	Positive line terminal
20	REG	Line voltage regulator decoupling
21	IR	Receive channel input
22	AGC	Automatic gain control
23	VDD	3.35 V supply voltage
24	MICS	Supply for electret microphones
25	STAB	Reference current adjustment
26	NC	no connect
27	VOL	Loudspeaker amplifier volume adjustment
28	TXOUT	Base microphone amplifier output
29	GATX	Base microphone gain adjustment
30	TXIN	Base microphone amplifier input
31	GNDTX	Ground reference for microphone amplifiers
32	MIC-	Inverting HS microphone input
33	MIC+	Non-inverting HS microphone input
34	DTMF	Dual Tone Multifrequency input
35	QR	Earpiece amplifier output
36	GARX	Earpiece amplifier gain adjustment
37	RECO	Receive amplifier output
38	HFTX	Input for auxiliary receive amplifier
39	HFC	Logic input
40	PD/	Power-down input

In fig. 1 it can be seen that the IC consists out of five main parts: the line interface, the supply block, the transmit block, the receive block with the loudspeaker amplifier and the logic block which controls the IC. These blocks are shortly described below including the function of the external components. The detailed description will follow in chapter 3.

Line interface :

The TEA1097 generates a stabilized voltage (called V_{ref}) between pins GND and SLPE. This reference voltage is line current dependant in order to get optimum supply for the loudspeaker amplifier and is stabilized by the capacitor C_{reg} connected at pin REG. The line current is sensed across the resistor connected between pins LN and SLPE.

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

An AGC function is provided when pin AGC is connected directly or through a resistor to LN.

The impedance of the apparatus is set by a network connected between LN and GND through a decoupling capacitor.

Supply:

The circuit can be supplied from the line and/or by an external supply. It provides a stabilized 3.35 V supply point for peripherals which can also be externally supplied in trickle mode. The TEA1097 can be switched into a low power consumption mode with the pin PD/.

Transmit:

The transmit signal can come from three preamplifiers: handset microphone (MIC+/MIC-), the auxiliary transmit (TXAUX) and the DTMF. The selection is made by the logic block. The signal reference is GNCTX, a "clean ground" which has to be connected to GND, for the base microphone. The inputs have to be coupled by means of capacitors. All the gains have a fixed value except the gain of the base microphone amplifier which is set with R_{gatx} .

Receive:

The signal received from the line is amplified from pin IR to pin RECO and/or to the auxiliary output AUXO. The input IR has to be coupled by means of a capacitor. From pin RECO, the signal is sent to the earphone amplifier at pins GARX and QR and to the input of the loudspeaker amplifier HFRX. The gain of the earphone amplifier is set with 2 resistors. From HFRX, the signal is sent to the loudspeaker amplifier (pins GALS and LSAO) and the volume can be adjusted by means of the potentiometer connected between input VOL and GNCTX, the gain of the loudspeaker amplifier is set by the resistor R_{gals} . The signal from the auxiliary input RAUX can also be sent to RECO.

Moreover the auxiliary output AUXO can get its signal from IR, MIC+/MIC- or HFTX.

Logic block :

The logic block manages the internal switches according to the following table.

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

LOGIC INPUTS					CONNECTIONS	APPLICATIONS
PD/	HFC	MUTT/	MUTR/	AUXC		
0	X	X	X	1	HFRX -> LSAO	Ring mode with SMPS
0	X	X	X	0		Flash, DC dialling
1	0	0	0	0	DTMF->LN ; CT->RECO (MICS, QR)	Tel. Set: DTMF dialling
1	0	0	1	0	MIC->AUXO; RAUX->RECO (MICS, QR)	Cordless intercom with handset; A.M.(record or listen with handset)
1	0	1	X	0	MIC->LN; IR->RECO; IR->AUXO MIC->TXOUT (MICS, QR)	Handset conversation; A.M. (record conv.)
1	0	1	0	1	TXAUX->LN ; IR->AUXO	Conversation with auxiliary (Fax, A.M., RF interface,..); Cordless: digital handsfree in mobile
1	1	0	1	1	RAUX->RECO; HFRX->LSAO	Listening on loudspeaker
1	1	0	0	1	TXAUX->LN ; IR->AUXO; RAUX->RECO; HFRX->LSAO	Answering Machine (outgoing message)
1	1	0	0	0	DTMF->LN ; CT->RECO; HFRX->LSAO (MICS, QR)	HF/GL Tel Set DTMF dialling
1	1	1	0	1	TXAUX->LN ; IR->AUXO; IR->RECO; HFRX->LSAO	Answering machine (incoming message); Fax with monitoring
1	1	0	1	0	TXIN->TXOUT; HFTX->AUXO; RAUX->RECO; HFRX->LSAO (MICS)	Cordless intercom with base; A.M. (record or listen with base)
1	1	1	1	0	TXIN->TXOUT; TXAUX->LN; IR->RECO; IR->AUXO; HFRX->LSAO (MICS)	Digital handsfree conversation; A.M. (record conv.)
1	1	1	0	0	MIC->LN; IR->RECO; IR->AUXO; HFRX->LSAO ; MIC->TXOUT (MICS,QR)	Group-listening conversation; A.M. (record conv.)

Fig. 3 Table of switch management

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

3. DESCRIPTION OF THE TEA1097

This chapter describes in detail the six blocks of the speech/handsfree circuit TEA1097: the line interface (3.1), the supply (3.2), the transmit block (3.3), the receive block (3.4) and the logic block (3.5). For each block the principle of operation is described and its adjustments and performances are discussed.

All values given in this chapter are typical and at room temperature unless otherwise stated. For more details, see TEA1097 device specification.

All the curves shown in this section result from measurement of typical samples using the schematic of fig. 57. All the component names refer to the basic application of the IC shown in appendix fig. 55.

3.1 Line interface

3.1.1 DC characteristics

Principle of operation

The TEA1097 generates a stabilized voltage (called V_{ref}) between pins GND and SLPE. This reference voltage, temperature compensated, is typically 3.7 V for line currents between 10 and 18 mA and 6.15 V for line currents between 46 and 140 mA. For line currents between 18 and 46 mA, V_{ref} increases proportionally to this line current with a slope of typically 87.5Ω so, from 3.7 to 6.15 V. The voltage at pin REG is used by the internal regulator to generate the stabilized V_{ref} voltage and is decoupled by a capacitor C_{reg} connected to LN.

For effective operation of the apparatus, the TEA1097 must have a low resistance to the DC current and a high impedance to speech signals. The C_{reg} capacitor, converted into an equivalent inductance (see "set impedance" section), realizes this impedance conversion from its DC value (R_{slpe}) to its AC value (Z_{imp} in the audio frequency range). The DC voltage between pins LN and SLPE is proportional to the line current.

This general configuration is shown in fig. 4.

**TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer**

Application Note

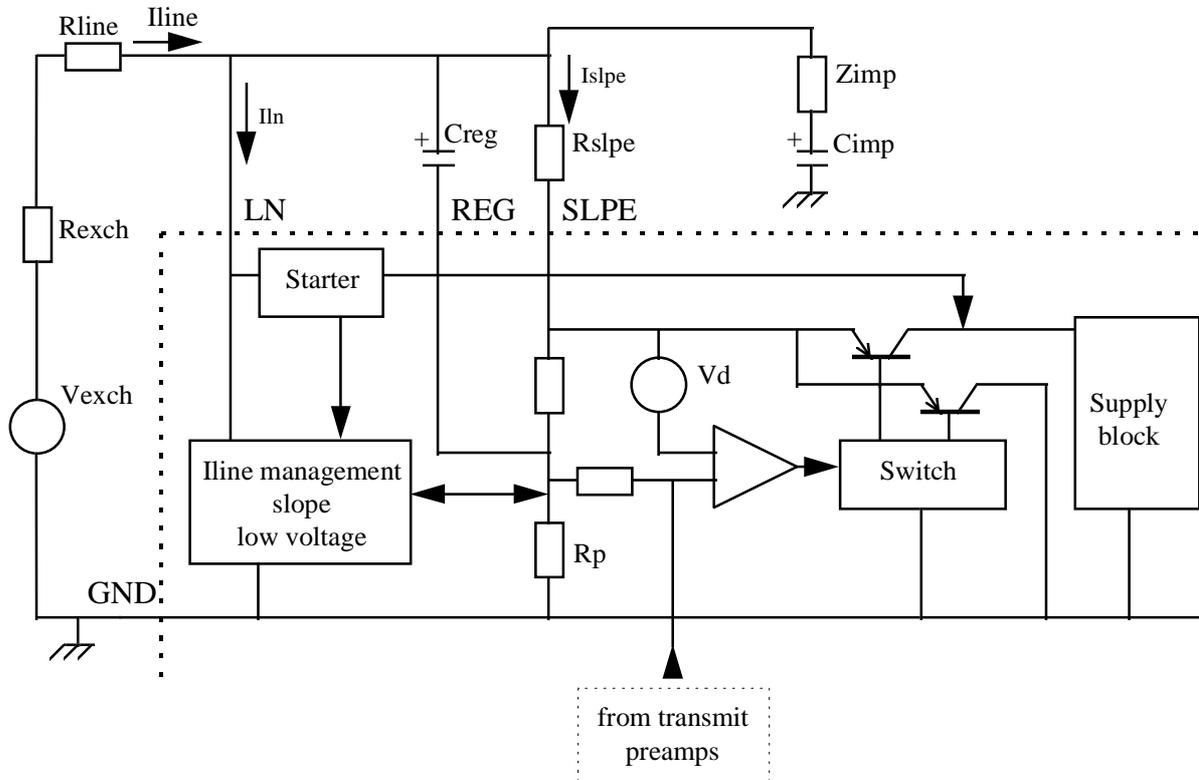


Fig. 4 DC characteristics configuration

The IC regulates the line voltage between pins GND and SLPE. The voltage on pin LN can be calculated as:

$$V_{ln} = V_{ref} + R_{slpe} \times I_{slpe}$$

$$I_{slpe} = I_{line} - I_{ln}$$

I_{line} = line current

I_{ln} = current consumption between LN and GND

Between 18 and 46 mA:

$$V_{ref} \cong 3.7 + (I_{slpe} - 18 \text{ mA}) \times 87.5$$

The DC line current I_{line} flowing into the apparatus is determined by the exchange supply voltage V_{exch} , the feeding bridge resistance R_{exch} , the DC resistance of the telephone line R_{line} and the voltage across the telephone set including diode bridge.

Below a threshold line current I_{th} (typically equal to 9 mA) the internal reference voltage (generating V_{ref}) is automatically adjusted to a lower value (down to an absolute minimum voltage of 1.6 V). This means that more sets can operate in parallel or that for very low voltage feeding bridge the line current has a higher value. For line currents below this threshold current, the TEA1097 has reduced sending and receiving performances. This is called the low voltage area.

The internal circuitry of the TEA1097 is supplied from pin VBB. In line powered application, this voltage is derived from the line voltage by the supply block and must be decoupled by a capacitor (C_{vbb}). Fig. 5 shows

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

the IC current consumption (I_{bb}) as a function of the VBB supply voltage in handset mode, DTMF mode and in digital handsfree mode.

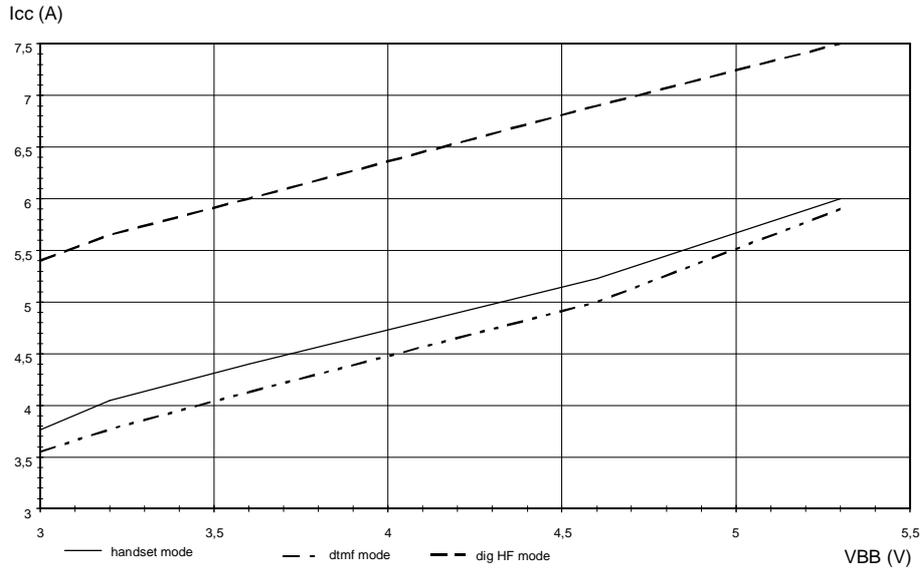


Fig. 5 I_{bb} versus V_{bb}

Fig. 6 shows the main voltages as a function of the line current in line powered conditions.

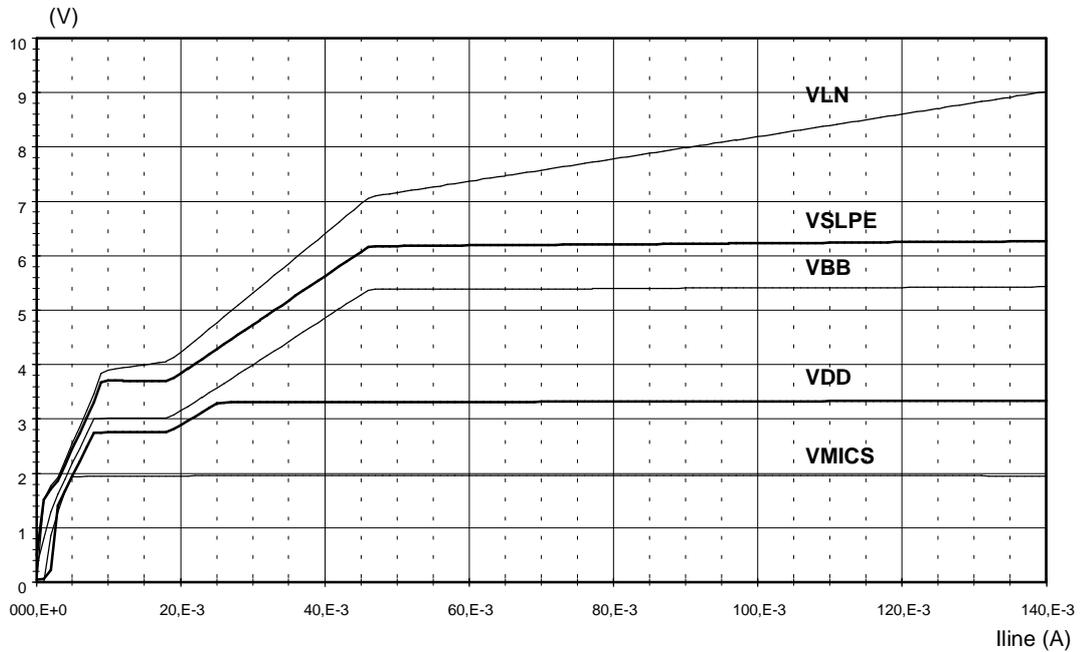


Fig. 6 Main voltages versus line current

**TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer**

Application Note

Fig. 7 shows the behavior in the low voltage area in line powered condition.

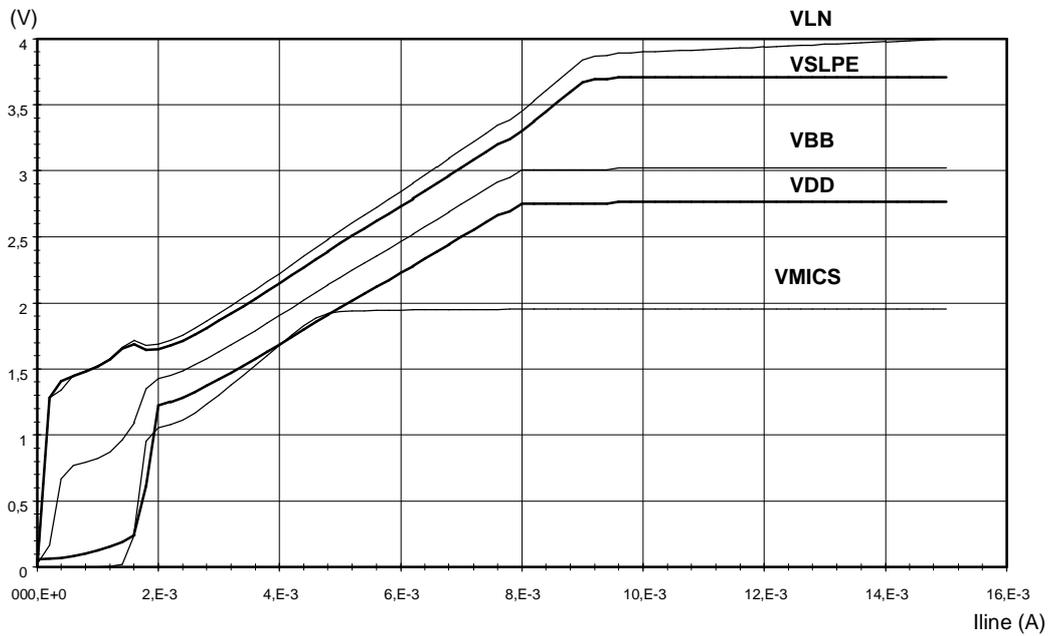


Fig. 7 Low voltage behavior in line powered condition

Fig. 8 shows the behavior in the low voltage area when VBB is externally supplied at 5 V.

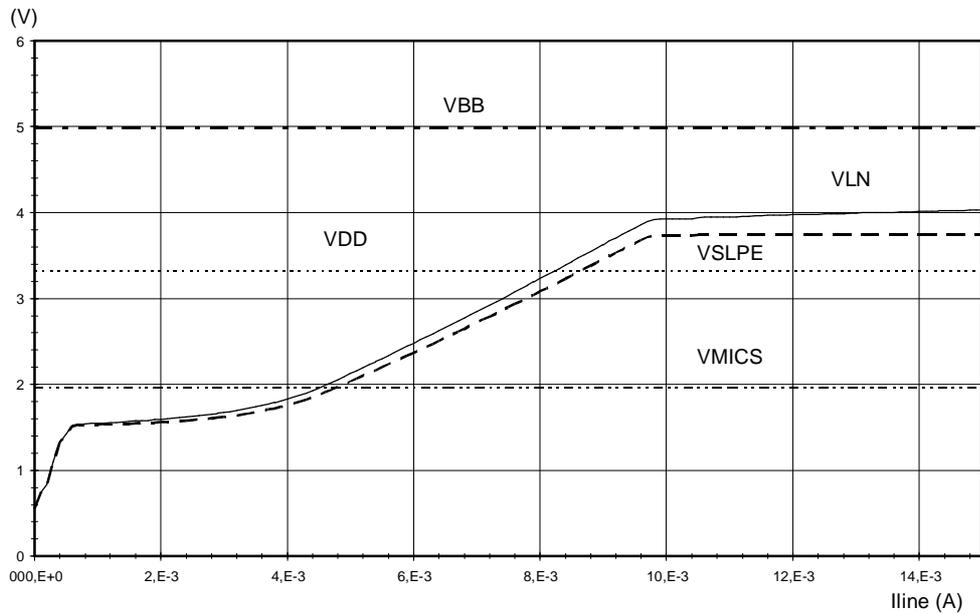


Fig. 8 Low voltage behavior when VBB = 5 V

**TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer**

Application Note

Adjustments and performances

The reference voltage, V_{ref} , can be adjusted by means of an external resistor R_{va} . It can be increased by connecting the R_{va} resistor between pins REG and SLPE (Fig. 9), or decreased by connecting the R_{va} resistor between pins REG and GND. In line powered application, it is possible to use the voltage reduction only for less than 300 mV because it reduces the VBB supply capability, this reduction is easier when VBB is provided by an external 5 V power supply. To ensure correct operation, it is not advised to adjust V_{ref} at a value lower than 3.3 V at 18 mA or higher than 7 V at a maximum line current of 90 mA (the maximum operating voltage of 12 V must be guaranteed by the application as well as the safe crystal operating temperature). These adjustments will slightly affect a few parameters: there will be a small change in the temperature coefficient of V_{ref} and a slight increase in the spread of this voltage reference due to matching between internal and external resistors. Furthermore, the R_{va} resistor connected between REG and GND will slightly affect the apparatus impedance (see section "set impedance").

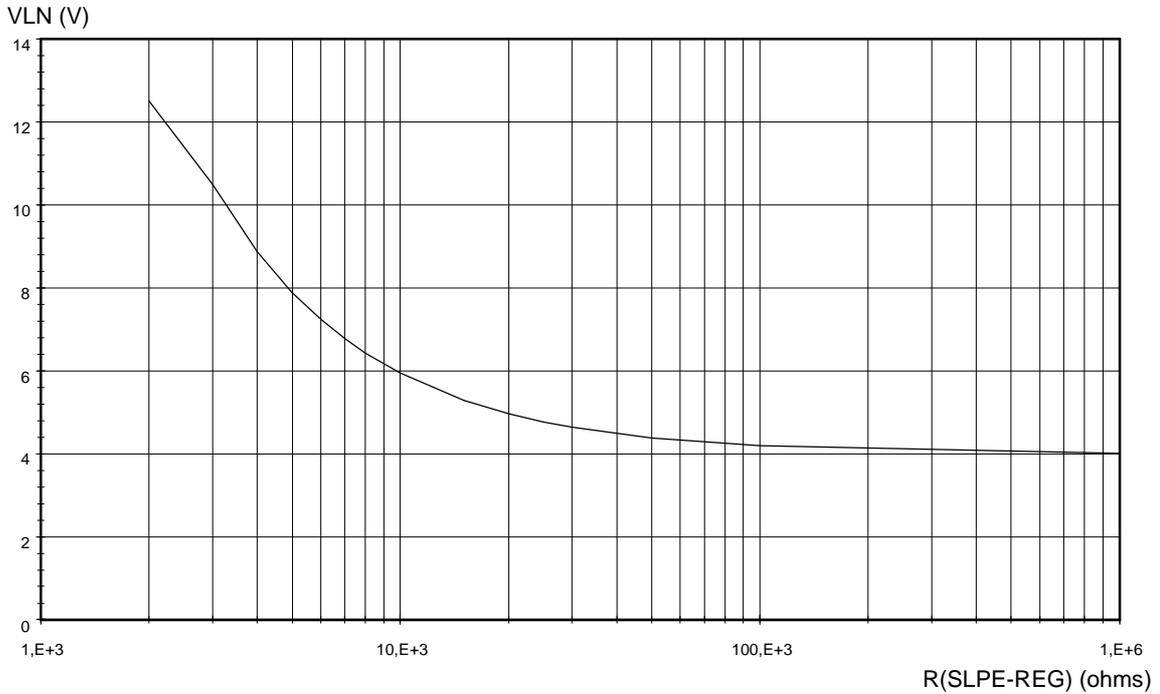


Fig. 9 Influence of the R_{va} resistor between REG and SLPE on V_{ln} at 15 mA

The DC slope of the voltage on pin LN is influenced by the R_{slpe} resistor as shown in fig. 10. This value of R_{slpe} may be slightly modified even if the preferred one is 20 Ω ; changing this value will affect more than the DC characteristics, it also influences the gains, the AGC characteristics, the maximum output swing on the line, the VBB slope start and stop currents and the low voltage threshold I_{th} .

TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer

Application Note

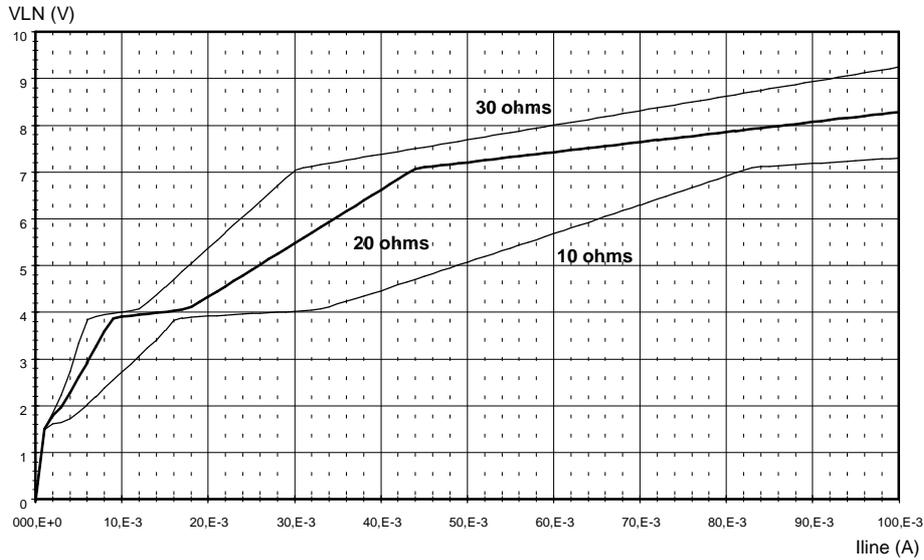


Fig. 10 Influence of Rslpe on the DC characteristics

3.1.2 Line impedance

Principle of operation

The TEA1097 behaves like an equivalent inductance that presents a low impedance to DC and a high impedance (Rp) to speech signals. Rp is an integrated resistance in the order of 25 kΩ +/-15%. It is in parallel with the external network realized by Zimp and Cimp. Thus, in the audio frequency range, the apparatus impedance (called set impedance) is mainly determined by the Zimp resistor. Fig. 11 shows an equivalent schematic for the set impedance.

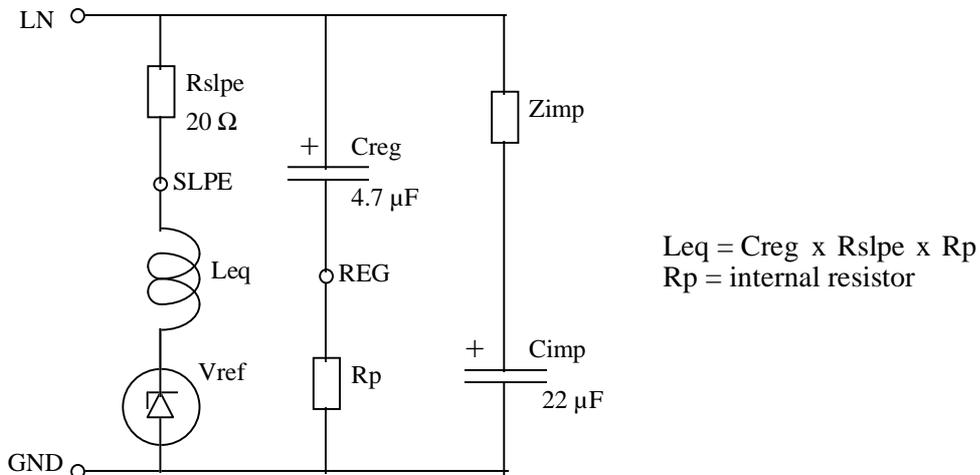


Fig. 11 Equivalent set impedance

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

Adjustments and performances

When decreasing the reference voltage V_{ref} , a resistor is connected between GND and REG in parallel of R_p (see fig. 11) so, slightly modifying the impedance.

If complex set impedance is required Z_{imp} is a complex network, if a purely resistive set impedance is required Z_{imp} is a resistor.

The value of the capacitor C_{imp} has to be high enough (advised value of $22 \mu F$) in order to have an impedance negligible compare to Z_{imp} or it may be used to generate the capacitive part of a complex impedance assuming that DC decoupling is kept.

3.1.3 Anti-sidetone network

Principle of operation

To avoid the microphone signal to come back with a too high level in the receive channel, the anti-sidetone circuit uses the microphone signal from pin SLPE (which is in opposite phase) to cancel the microphone signal at the IR input of the receive amplifiers. The anti-sidetone bridge principle already used for the TEA106x or the TEA111x families is used in a reversed way for the design of the anti-sidetone network as shown in fig. 12.

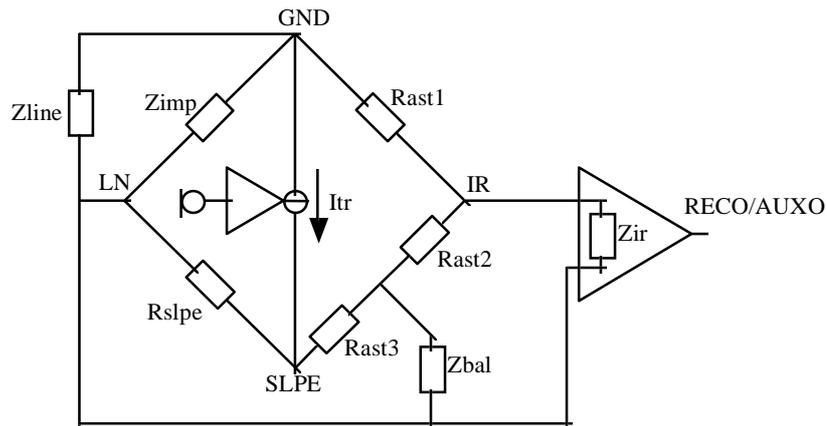


Fig. 12 Anti-sidetone bridge connection

This anti-sidetone bridge has the advantage of a relative flat transfer function in the audio frequency range between the line and the outputs RECO or AUXO, both with real and complex set impedances. Furthermore, the attenuation of the bridge for the receive signal (between pins LN and IR) is independent of the value chosen for Z_{bal} after the set impedance has been fixed and the condition shown in equation (st) is fulfilled. Therefore, readjustment of the overall receive gain is not necessary in many cases.

The anti-sidetone circuit is composed of: Z_{imp}/Z_{line} , R_{ast1} , R_{ast2} , R_{ast3} , R_{slpe} and Z_{bal} . Maximum compensation is obtained when the following conditions are fulfilled:

$$R_{slpe} \times R_{ast1} = Z_{imp} \times (R_{ast2} + R_{ast3}) \tag{st}$$

$$k = [R_{ast2} \times (R_{ast3} + R_{slpe})] / (R_{ast1} \times R_{slpe})$$

$$Z_{bal} = k \times Z_{line}$$

The scale factor k is chosen to meet the compatibility with a standard value of capacitor for Z_{bal} .

with auxiliary inputs/outputs and analog multiplexer

In practice, Z_{line} varies strongly with line length and line type. Consequently, the value for Z_{bal} has to be chosen to fit with an average line length giving acceptable sidetone suppression with short and long lines. The suppression further depends on the accuracy with which Z_{bal} equals this average line impedance.

Example

Let's optimize for a theoretical equivalent average line impedance shown in Fig. 13.

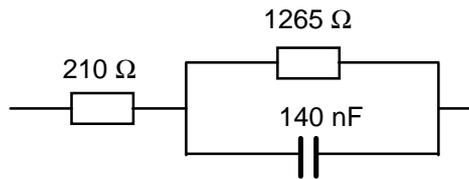


Fig. 13 Equivalent average line impedance

For compatibility of the capacitor value in Z_{bal} with a standard capacitor value from the E6 series (220 nF):

$$k = 140 / 220 = \mathbf{0.636}$$

For R_{ast2} , a value of 3.92 kΩ has been chosen. So, using the previous equations, we can calculate Z_{bal} , R_{ast1} , R_{ast3} . We find $R_{ast1} = 130 \text{ k}\Omega$, $R_{ast3} = 390 \Omega$, and for Z_{bal} **130 Ω in series with 220 nF // 820 Ω**.

The attenuation of the receive line signal between LN and IR can be derived from the following equation:

$$V_{ir} / V_{in} = (Z_{ir} // R_{ast2}) / [R_{ast1} + (Z_{ir} // R_{ast2})]$$

If $R_{ast2} \gg (R_{ast3} // Z_{bal})$.

With the values used in this example, it gives 32 dB at 1 kHz.

Z_{ir} is the receive amplifier input impedance, typically 20 kΩ.

3.1.4 Automatic gain control

Principle of operation

The TEA1097 performs automatic line loss compensation. According to the line DC current, the automatic gain control varies the gains of the amplifiers MIC+/- to LN, TXAUX to LN, IR to RECO and IR to AUXO. To enable this AGC function, the pin AGC must be connected to the pin LN. For line currents below a current threshold, I_{start} (typically 23mA), the gain control factor α is equal to 1, giving the maximum value to the gains. If this threshold current is exceeded, the gain control factor α is reduced and then the gains of the controlled amplifiers are also reduced. When the line current reaches an other threshold current, I_{stop} (typically 57 mA), the gain control factor α is limited to its minimum value equal to 0.49 or 0.47, giving the lower value to the transmit and receive controlled gains. The gain control range of these amplifiers is typically 6.2 dB or 6.6 dB depending on the amplifier (see datasheet), which corresponds approximately to a line length of 5.5 km (0.5 mm twisted pair copper) with an attenuation of 1.2 dB/km.

The attenuation is correlated to the current I_{lagc} sunk at pin AGC: when this current is lower than typically 4.8 μA the gains are maximum, when this current is higher than typically 12 μA the gains are minimum. This current is proportional to the voltage between pins SLPE and LN. There is an internal resistor which sets I_{start} and I_{stop} , adding R_{agc} externally in series (between pins AGC and LN) reduces I_{lagc} and increases the values of I_{start} and I_{stop} .

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

Adjustments and performances

The AGC of the TEA1097 can be used with different exchange supply voltages and different feeding bridge resistances. For this purpose, a resistor R_{agc} , can be inserted between pins AGC and LN. This R_{agc} resistor increases the two threshold currents I_{start} and I_{stop} . Fig.14 shows the control of the microphone gain versus the line current for two values of R_{agc} . When no AGC function is required, the AGC pin must be left open, then the control factor α equals to 1 and all controlled gains are at their maximum values.

When $R_{agc} = 0$ and the value of I_{start} is too high, increasing slightly the value of R_{slpe} reduces proportionally I_{start} and shifts the AGC to lower currents but the gains, the DC characteristic and the value of V_{BB} are also modified. If the value of R_{slpe} has to be increased, it is possible to restore the typical gains (but not the value of V_{BB}) by connecting in parallel an RC series network which makes a total AC impedance of 20Ω .

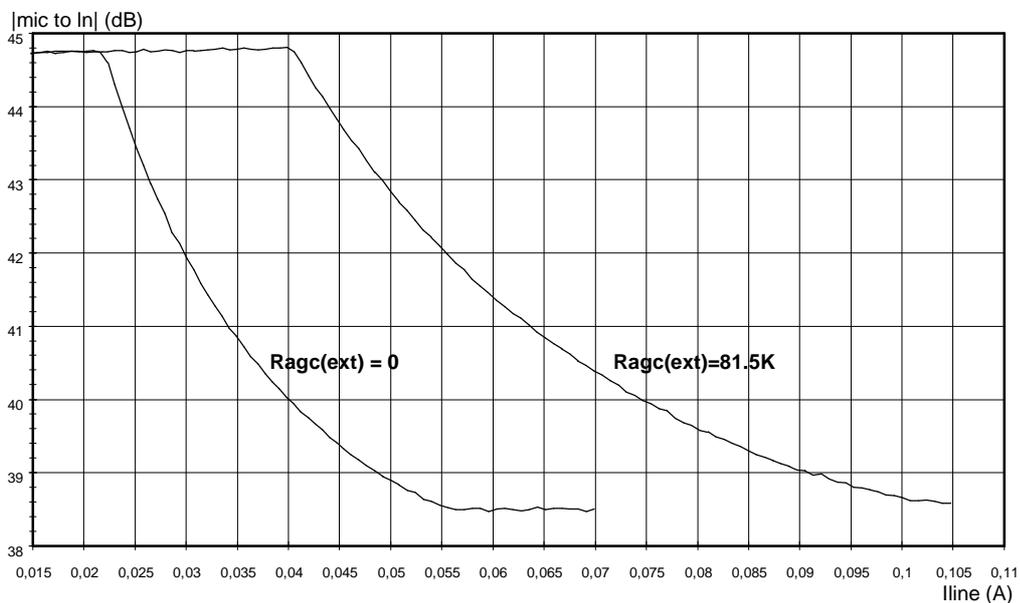


Fig. 14 AGC on the microphone gain versus line current and R_{agc}

3.2 Supplies

The TEA1097 provides three supply points, V_{BB} is the strong supply for most of the internal circuitry and the amplifiers, V_{DD} is a 3.35 V supply for the dialler or the microcontroller and $MICS$ is a switched supply point for the electret microphones. Moreover, the TEA1097 can be powered by an external power supply connected at the input ESI .

Fig. 15 shows the block diagram of the supply block:

TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer

Application Note

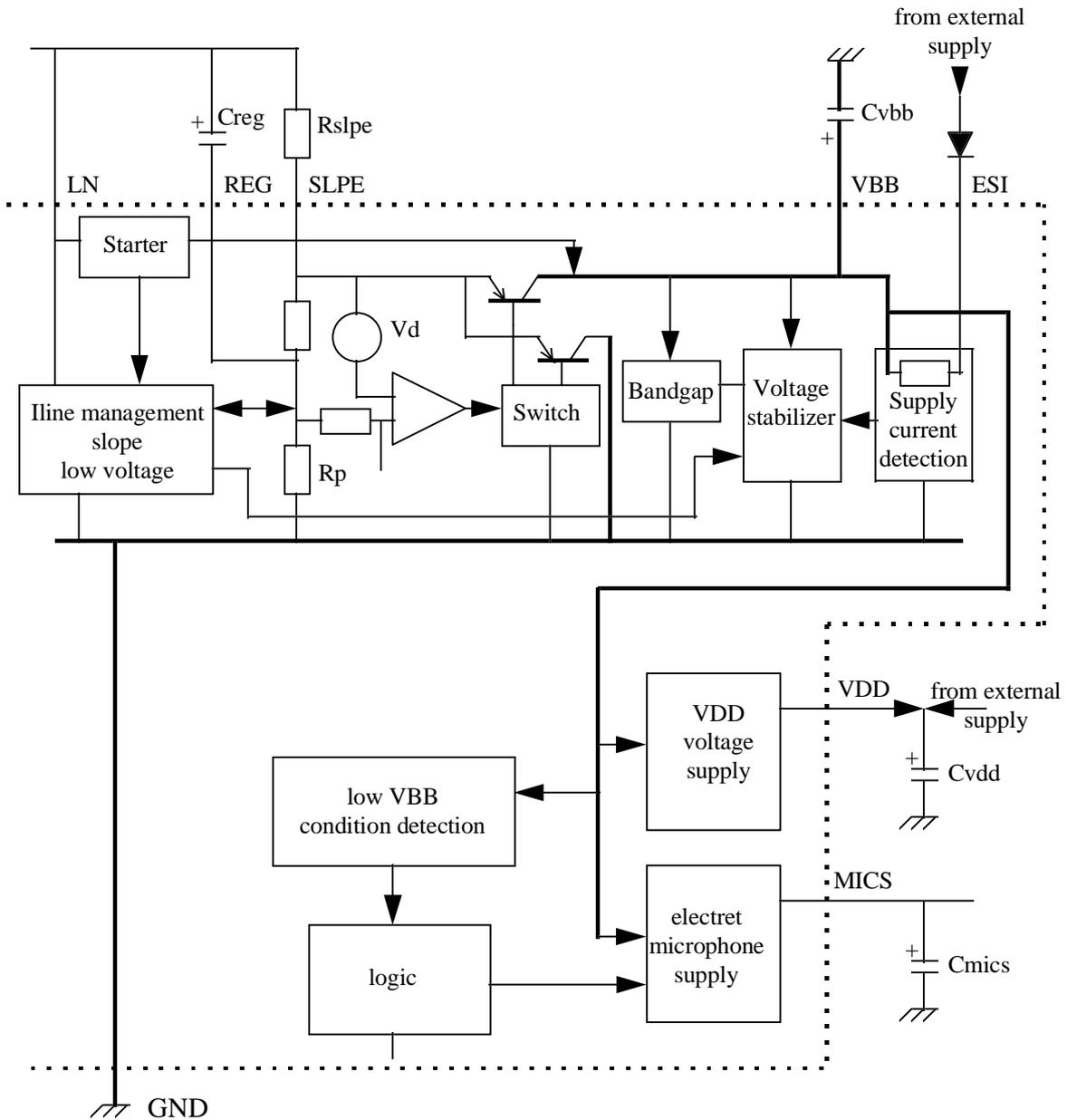


Fig. 15 Block diagram of the supply block

3.2.1 Supply VBB

Principle of operation

VBB can be either line powered or externally powered at ESI, when both supplies are available, the strongest of the two is automatically selected and used internally. When VBB is purely line powered, its value is correlated with the value of the line voltage and then of the line current as follows:

- below 9 mA : low voltage area

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

- 9 to 18 mA : VBB = 3 V
- 18 to 46 mA : VBB increases with a slope of 84 Ω from 3 to 5.35 V
- above 46 mA : VBB = 5.35 V

The correlation between line voltage and VBB is done in order to get a voltage difference between Vslpe and VBB of at least 0.7 V in order to guarantee a good power supply efficiency when AC signal is present on SLPE. On the block diagram, two PNP transistors drive the line current either to VBB or to GND: when the voltage on SLPE is higher than VBB + 0.3 V the current is driven to VBB, when the voltage on SLPE is lower than VBB the line current is driven to GND, when the voltage on SLPE is between VBB and VBB + 0.3 V both transistors are conducting in order to minimize distortion.

The correlation between line voltage and line current is done in order to get the optimized correlation between the power that can be extracted from the line and the power that can be delivered to the loudspeaker amplifier.

Fig. 6 shows these different voltages versus line current, fig. 16 shows the output level power on different loads in series with 220 μF versus input voltage at ESI.

Pmax for 2% thd on LSAO

(mW)

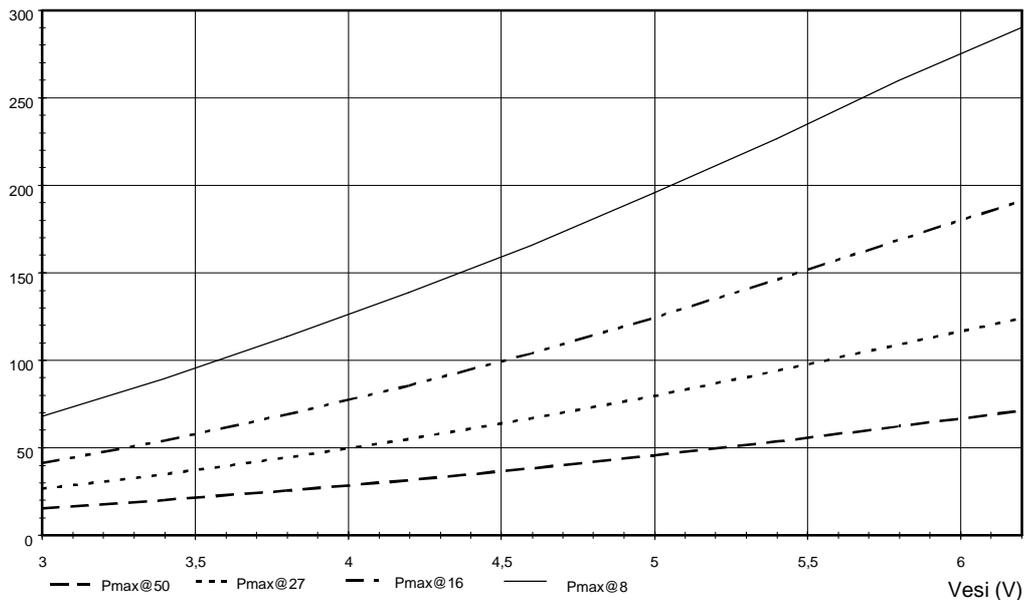


Fig. 16 Loudspeaker output power versus input voltage at ESI

The block diagram of Fig. 15 shows that an external power supply can be connected at ESI, the supply current detection block controls the selection of the supply used by sensing the current in a serial resistor. When the current is flowing from SLPE to VBB line current is used as power source, when current is flowing from ESI to VBB the external supply is then used and the shunt regulator built in the voltage stabilizer is adjusted to the external source (clamping VBB at 6.6 V) in order to get the value of VBB as close as possible to ESI value without extra current consumption. This shunt regulator is switched-off in power-down mode only and is still available in ringer mode.

TEA1097 Speech and loudspeaker amplifier IC**Application Note****with auxiliary inputs/outputs and analog multiplexer**

A “low VBB condition detection” block detects if the value of VBB becomes higher than 2.9 V. The logic block is enabled when VBB becomes higher than 2.9 V. The loudspeaker amplifier parts are enabled when VBB becomes higher than 2.9 V.

When VBB becomes lower than 2.7 V, the VBB detector of the dynamic limiter on LSAO discharges the capacitor at pin DLC and the loudspeaker amplifier is disabled.

This block detects also if VBB becomes lower than 2.5 V. When VBB becomes lower than 2.5 V, the logic block is disabled and the handset speech mode is forced. Moreover, the loudspeaker amplifier are disabled.

The difference between 2.5 V and 2.9 V make hysteresis in order to keep stable behaviors.

VBB can be used to supply external circuits, in line powered condition the total amount of current drawn from VBB, MICS and from VDD must be low enough to stay compatible with the value of the line current.

A “starter” block is included in order to speed-up the charge of the capacitor Cvbb. This starter is active as soon as some voltage is available on the line when VBB is still lower than 2.4 V; when VBB is decreasing, it becomes active again when VBB becomes lower than 1.9 V.

Adjustments and performances

A capacitor Cvbb must be connected between pins VBB and GND, the advised value is 470 μ F, a higher value would delay the start-up time of the system.

When an external voltage source is provided at ESI, a diode is necessary in order to allow VBB to take a value higher than the value of this source when the line current is high enough (e.g. 3.3 V at ESI and >46 mA of line current which provides VBB at 5.35 V) and to prevent VBB from collapse if this supply is temporarily out of order.

If an Rva resistor is connected between REG and GND to reduce the line voltage, the 0.7 V voltage difference between SLPE and VBB is reduced, then the power available for the loudspeaker amplifier is dramatically reduced and even can't exist if the remaining voltage is lower than 0.3 V.

The “low VBB condition detector” enables the loudspeaker amplifier and the logic block when VBB becomes higher than 2.9 V. The loudspeaker amplifier is disabled when VBB falls down below 2.7 V while the logic block is disabled when VBB falls down below 2.5 V. When VBB has fallen below 2.5 V, in order to indicate that the handset conversation mode is forced, the pin HFC is pulled to GND.

These hysteresis allow a stable operation of the loudspeaker amplifier in low supply condition because, if there is no change in the supply condition, the dynamic limiter should avoid VBB to fall below 2.7 V.

Fig. 17 shows the current consumption on VBB in ringer mode when no signal is sent to the loudspeaker amplifier and the input current on ESI necessary to get this value of VBB. The difference between these currents is available as power for the loudspeaker amplifier.

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

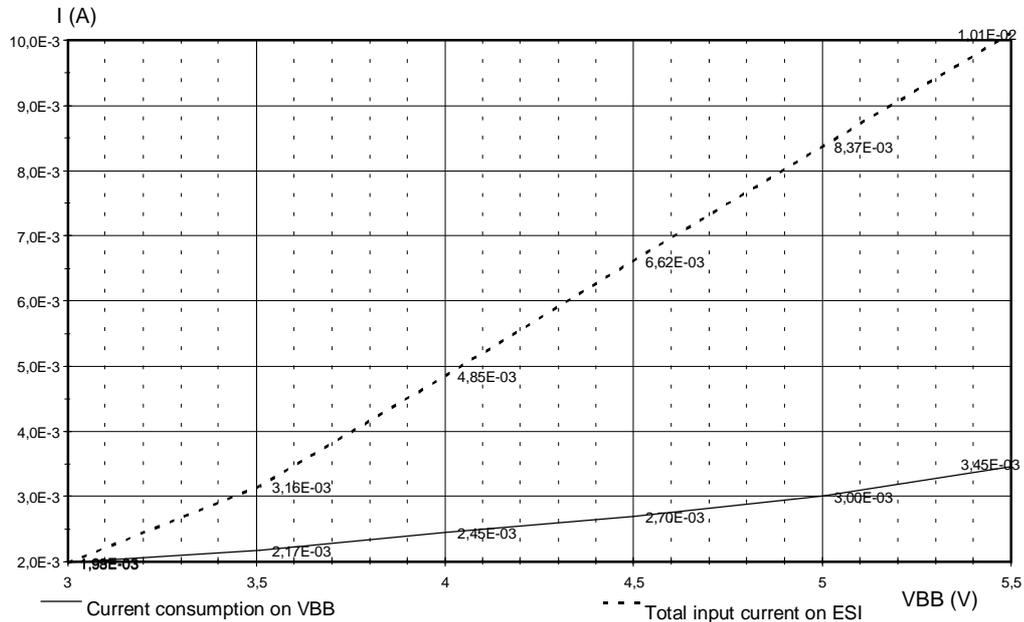


Fig. 17 Current consumption on VBB in "ring mode" versus VBB

3.2.2 Supply VDD

Principle of operation

The supply block VDD is fed from VBB, so VDD is typically 0.25 V lower than VBB and clamped typically at 3.35 V. Nevertheless the block VDD can be externally supplied, if the external source provides a current lower than 60 μ A, VDD is also clamped at 3.35 V, if this current is higher than 200 μ A the voltage on VDD follows the voltage of the external source. These two modes allow either the supply of a microcontroller with a trickle current without any additional zener diode or the supply from an external regulated power supply without too much current consumption.

The output capability of VDD is typically 3 mA when ESI is supplied or when the line current is higher than 11 mA (with no extra consumption on VBB) in line powered mode. In line powered mode, this output capability is reduced progressively down to about 1 mA at 7 mA of line current, depending on the current drawn at MICS.

In power down or ringer modes, VDD regulator is still working and provides 3.35 V as long as VBB is higher than 3.65 V. Moreover, the current consumption of VDD is lower than 150 nA when $VDD \leq 1.5$ V in order to allow supply of the dialler or microcontroller with a trickle current.

Adjustments and performances

A capacitor Cvdd must be connected between pins VDD and GND even if this output is not functionally used; in order to keep a small start-up time, its value must be limited to a few 10 μ F. In power down mode (DC dialling or flash) the block VDD is still supplied from VBB and the capacitor Cvbb is the main tank.

When an external voltage source is provided, a diode in series is mandatory if this source is lower than 3.5 V or if it may be switched-off. If it is higher than 3.5 V the current consumption is less than 200 μ A.

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

Fig. 18 shows the typical current consumption on VDD in trickle mode when VBB = 0.

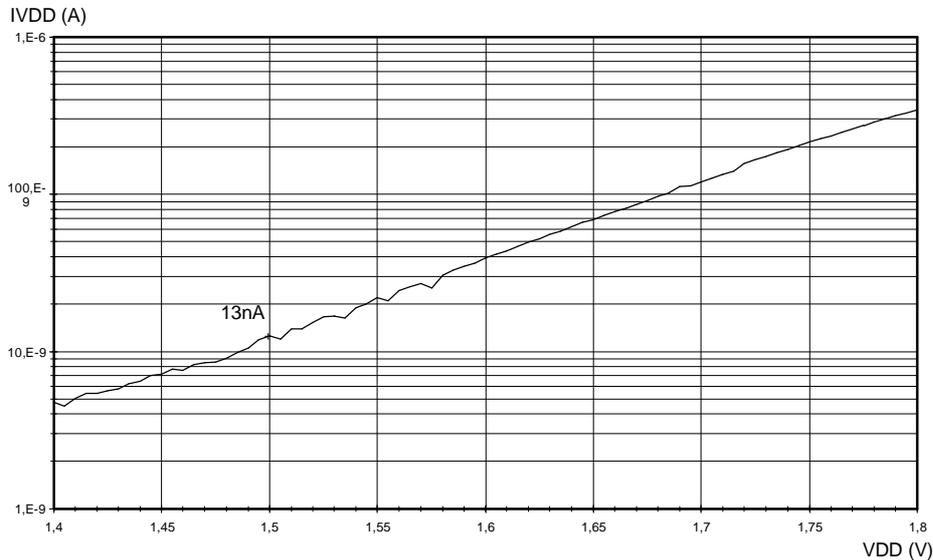


Fig. 18 Current consumption on VDD at VBB = 0

3.2.3 Microphone supply MICS

Principle of operation

The electret microphone supply block is fed from VBB and provides a 2 V regulated supply with a capability of 1 mA. The output impedance is typically 200 Ω and must be filtered with a capacitor referenced to GNDTX. This output is switched-off in power down mode and in modes where the electret microphones are not necessary (see list in fig. 3).

Adjustments and performances

When the output is filtered with a 10 μF capacitor to GNDTX, the noise at MICS is typically -114 dBVp. The value of this capacitor fixes the impedance of this supply point; when the value of this capacitor is too small, the attenuation of the handset microphone signal may not be sufficient.

3.3 Transmit

The selection of the signal transmitted on line is made according to the table of fig. 3. This signal comes from the four following amplifiers: handset microphone amplifier, DTMF amplifier, base microphone channel and auxiliary transmit amplifier.

Fig. 19 shows the block diagram of the transmit part.

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

The microphone amplifier has symmetrical high input impedances (typically 70 k Ω -2 times 35 k Ω - between pins MIC+ and MIC- with maximum tolerances of +/- 15%).

As can be seen from fig. 19, the microphone amplifier to LN is built up out of two parts: a preamplifier which realizes a voltage to current conversion, and an end-amplifier (common with the other three transmit paths) which realizes the current to voltage conversion. The overall gain $G_{v(\text{mic-ln})}$ of the microphone amplifier from inputs MIC+/MIC- to output LN is internally set and given by the following equation:

$$G_{v(\text{mic-ln})} = 20 \times \log A_{\text{vmic}}$$

$$A_{\text{vmic}} = 5.7 \times (R_{\text{gasint}} / R_{\text{refint}}) \times (R_i / Z_l / R_{\text{slpe}}) \times \alpha$$

with:

R_i = the AC apparatus impedance, R_{cc}/R_p (typically 620 Ω // 25 k Ω)

R_{gasint} = internal resistor realizing the current to voltage conversion (typically 27.6 k Ω with a spread of +/-15%)

R_{refint} = internal resistor determining the current of an internal current stabilizer (typically 14.7 k Ω with a spread of +/- 15% correlated to the spread of R_{gasint})

Z_l = load impedance of the line during the measurement

α = gain control factor varying from 1 at $I_{\text{line}} = 15$ mA to 0.49 at $I_{\text{line}} = 70$ mA when AGC function is applied (see chapter 3.1.4 for details)

Using these typical values in the equation and assuming $Z_{\text{line}} = 600$ Ω , we find a gain equal to:

$$G_{v(\text{mic-ln})} = 20 \times \log A_{\text{vmic}} = 44.1 \text{ dB} \quad \text{at } I_{\text{line}} = 15 \text{ mA}$$

The AGC gain control acts on the microphone preamplifier stage, modifying its transconductance. Moreover the logic block enables or disables the preamplifier according to the selected mode (see fig. 3).

The inputs are biased at one V_d . The input of this microphone amplifier is able to handle AC signals up to 18 mV_{rms} with less than 2% total harmonic distortion.

The microphone amplifier to TXOUT is used for monitoring the microphone signal in order to build an external antihowling circuit (§3.4.5). It is also built up out of two parts: a preamplifier which realizes a voltage to current conversion, and an end-amplifier (common with the handsfree microphone amplifier) which realizes the current to voltage conversion. The overall gain $G_{v(\text{mic-txout})}$ of the microphone amplifier from inputs MIC+/MIC- to output TXOUT is fixed and given by the following equation:

$$G_{v(\text{mic-txout})} = 20 * \log (6.4 * R_{\text{gatxint}} / R_{\text{rint}}).$$

R_{gatxint} = internal resistor (typically 80 k Ω with a spread of +/-15%)

R_{rint} = internal resistor (typically 1.66 k Ω with a spread of +/-15%)

Adjustments and performances

Fig. 20 shows the typical frequency response of the microphone amplifier of the TEA1097.

**TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer**

Application Note

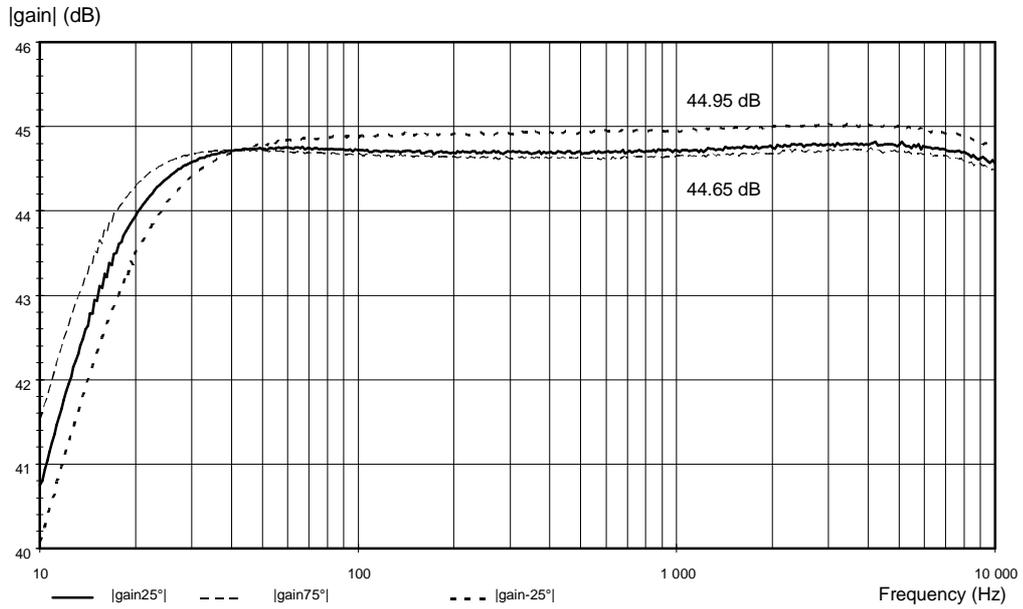


Fig. 20 Handset microphone gain versus frequency: influence of temperature

Fig. 21 shows the distortion of the signal on the line as a function of the microphone signal at nominal DC settings and for a different line currents.

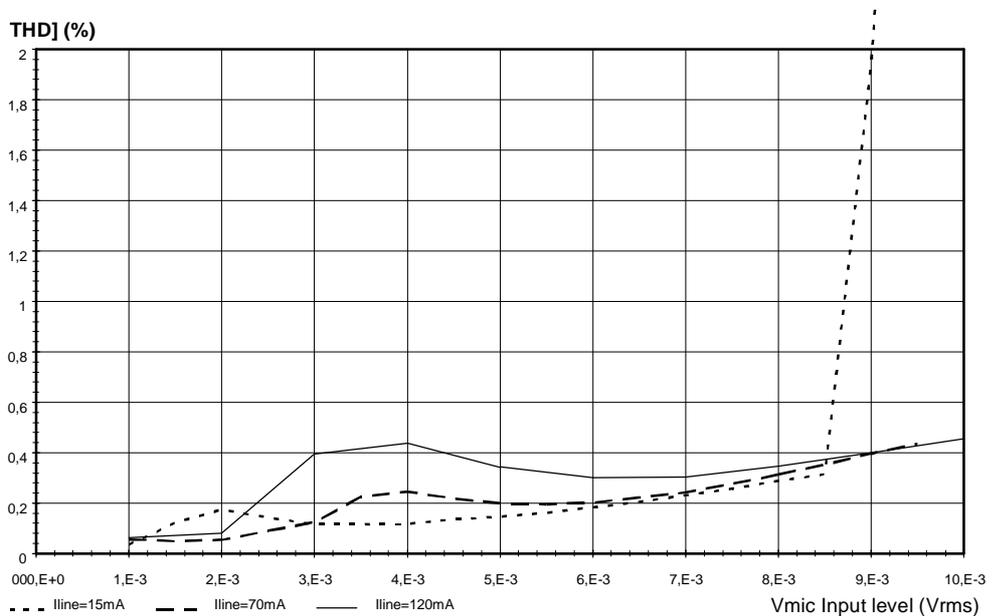


Fig. 21 Distortion on line versus handset microphone signal on TEA1097

**TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer**

Application Note

Fig. 22 shows the distortion of the line signal versus level at line current of 4 mA.

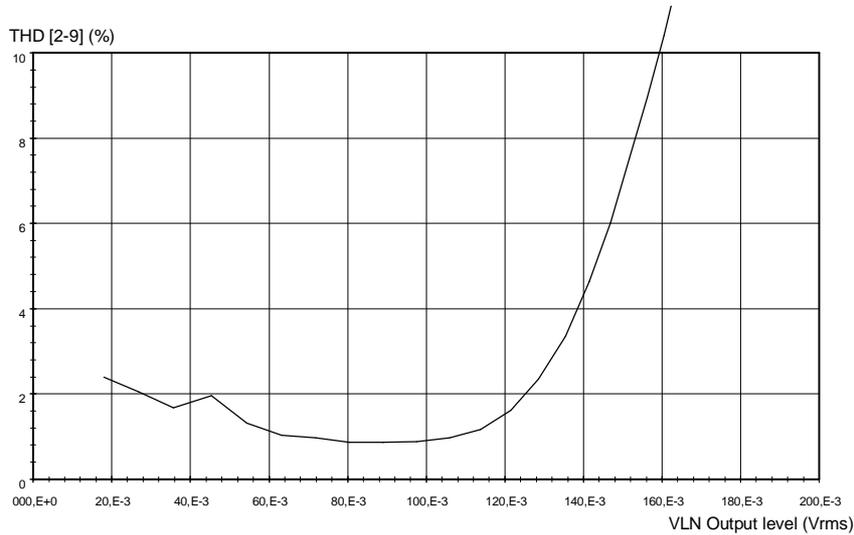


Fig. 22 Distortion of line signal at I_{line} = 4 mA

Fig. 23 shows the microphone noise (psophometrically weighted: P53 curve) versus line current when a 200 Ω resistor is connected between the inputs MIC- and MIC+.

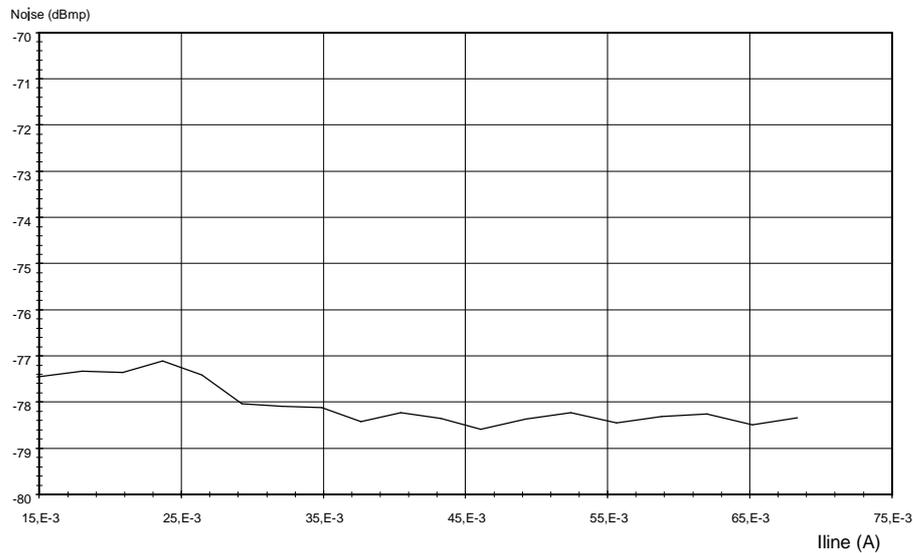


Fig. 23 Handset microphone noise versus line current

Fig. 24 shows the common mode rejection ratio at 15 mA. Two curves are present in this fig. 24, the first one is the spectrum of the signal on pin LN when a microphone signal is applied on pin MIC- while pin MIC+ is shorted to GND, the second one is the spectrum of the signal on pin LN when a microphone signal is applied on pins

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

MIC- and MIC+ shorted together. Both signals are at 1 kHz, the difference between the two curves gives the CMRR.

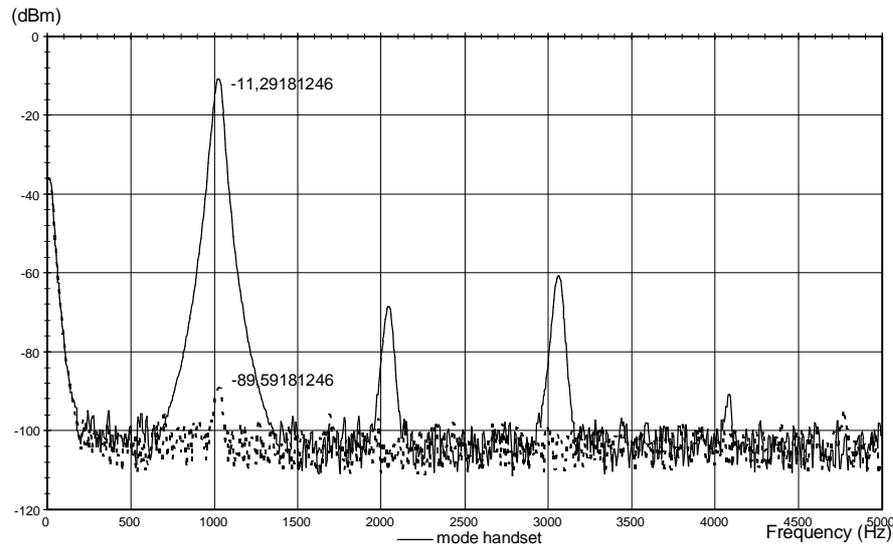


Fig. 24 Common mode rejection ratio on microphone

3.3.2 DTMF amplifier

Principle of operation

The DTMF amplifier has an a-symmetrical high input impedance of 20 k Ω between pins DTMF and GND with a maximum spread of +/-15%. The input is biased at GND, so if the input signal is polarized at GND there is no need of decoupling capacitor in series. The DTMF amplifier is built up out of three parts: an attenuator by a factor of 7.15, a preamplifier which realizes the voltage to current conversion and the same end-amplifier as the handset microphone amplifier. No AGC is applied to the DTMF channel. The overall gain $G_v(\text{dtmf-In})$ of the DTMF amplifier from input DTMF to output LN is given by the following equation:

$$G_v(\text{dtmf-In}) = 20 \times \log A_{\text{vmf}}$$

$$A_{\text{vmf}} = 0.66 \times (R_{\text{gasint}} / R_{\text{refint}}) \times (R_i // Z_l / R_{\text{slpe}})$$

with:

R_i = the AC apparatus impedance, $R_{\text{cc}}//R_p$ (typically 620 Ω // 25 k Ω)

R_{gasint} = internal resistor realizing the current to voltage conversion (typically 27.6 k Ω with a spread of +/-15%)

R_{refint} = internal resistor determining the current of an internal current stabilizer (typically 14.7 k Ω with a spread of +/- 15% correlated to the spread of R_{gasint})

Z_l = load impedance of the line during the measurement

Using these typical values in the equation and assuming $Z_{\text{line}} = 600 \Omega$, we find a gain equal to:

$$G_v(\text{dtmf-In}) = 20 \times \log A_{\text{vmf}} = 25.4 \text{ dB}$$

**TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer**

Application Note

Fig. 25 shows the frequency response of the DTMF amplifier at 15 mA and different temperatures.

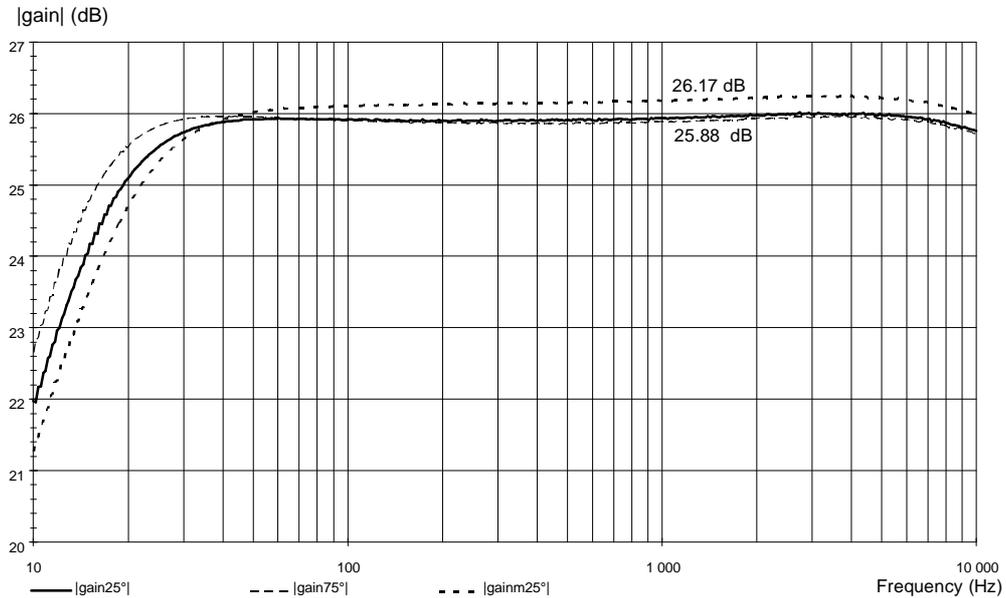


Fig. 25 DTMF gain versus frequency: influence of the temperature

The input of the DTMF amplifier can handle signals up to 180 mVrms with less than 2% THD. Fig. 26 shows the distortion on line versus the rms input signal at different line currents.

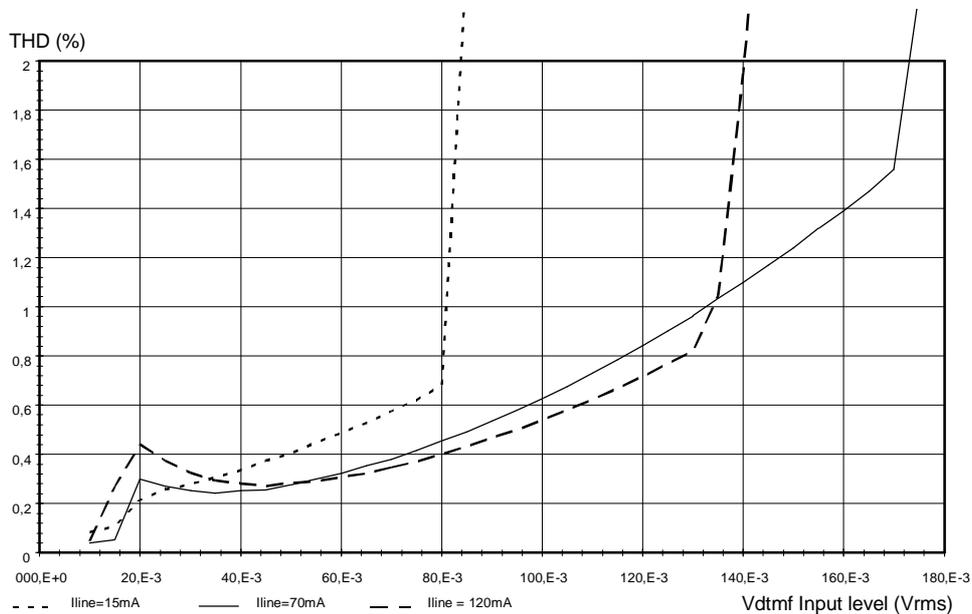


Fig. 26 Distortion of the DTMF signal on line versus input signal

**TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer**

Application Note

3.3.3 Base microphone amplifier

Principle of operation

The base microphone amplifier is referenced to pin GNDTX. This is in order to prevent interference from other blocks of the TEA1097 or of the application, GNDTX is called a clean ground. The input and output signals of the microphone channel have to be referenced to GNDTX. Pin GNDTX itself has to be shorted to GND.

The input of the base microphone amplifier is pin TXIN. It is an a-symmetrical input well suited for electret microphones. Induced signals in the short wire between the microphone and pin TXIN are assumed to be negligible. This is in contrary with the handset microphone which is connected via the handset cord.

The output of the microphone amplifier is pin TXOUT. In digital handsfree mode, pin TXOUT has to be connected via a decoupling capacitor to the input of the codec.

As can be seen in fig. 19, between pins TXIN and TXOUT, this microphone amplifier is built up out of two parts: a preamplifier and an end-amplifier. The gain of the end-amplifier is determined by the external feedback resistor Rgatx.

The overall gain $G_v(txin-txout)$ of the microphone amplifier from input TXIN to output TXOUT is given as:

$$G_v(txin-txout) = 20 * \log (0.7 * R_{gatx} / R_{stab}).$$

With Rstab being the resistor at pin STAB of 3.65 kΩ.

Adjustments and performances

A base microphone, referenced to GNDTX, can be connected to the input TXIN via a DC blocking capacitor Ctxi. Together with the input impedance at pin TXIN of 20 kΩ, this capacitor form a first order high-pass filter which can be used to adjust the transmit curve.

The base electret microphone can be supplied from MICS via a resistor.

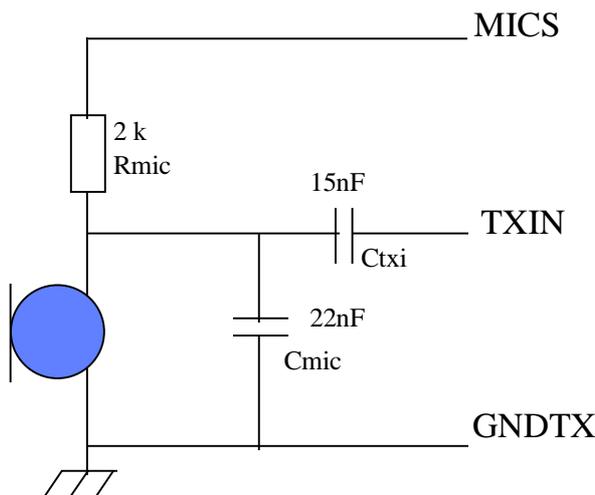


Fig. 27 Connection of the handsfree electret microphone

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

The sensitivity of the electret microphone is set via resistor R_{mic} . By putting a capacitor C_{mic} in parallel with the microphone, a first order low-pass filter is formed for the microphone signal in order to adjust the transmit curve.

Via the resistor R_{gatx} , the gain of the microphone amplifier can be adjusted from +6 to +31 dB to suit application specific requirements. With the resistor $R_{gatx} = 30 \text{ k}\Omega$, the gain equals typically 15 dB.

Capacitor C_{gatx} can be applied in parallel with resistor R_{gatx} to provide a first order low-pass filter for the adjustment of the transmit curve.

The input of the microphone amplifier can handle signals up to 18 mVrms with 2% total harmonic distortion.

The TXOUT output of the TEA1097 has an internal impedance of 200Ω and its output drive capability is $20 \mu\text{Arms}$.

The output noise at TXOUT of the TEA1097 is -103 dBVp (psophometrically weighted) at a gain of 15 dB.

3.3.4 Auxiliary transmit amplifier TXAUX

Principle of operation

The auxiliary transmit amplifier has an a-symmetrical high input impedance of $20 \text{ k}\Omega$ between pins TXAUX and GND with a maximum spread of +/-15%. The auxiliary transmit amplifier is built-up out of two parts: a preamplifier which realizes the voltage to current conversion and the same end-amplifier as the handset microphone amplifier. The overall gain $G_v(\text{txaux-ln})$ of the auxiliary transmit amplifier from input TXAUX to output LN is given by the following equation:

$$G_v(\text{txaux-ln}) = 20 \times \log A_{vtxa}$$

$$A_{vtxa} = 0.151 \times (R_{gasint} / R_{refint}) \times (R_i // Z_l / R_{slpe}) \times \alpha$$

with:

R_i = the AC apparatus impedance, $R_{cc} // R_p$ (typically $620 \Omega // 25 \text{ k}\Omega$)

R_{gasint} = internal resistor realizing the current to voltage conversion (typically $27.6 \text{ k}\Omega$ with a spread of +/-15%)

R_{refint} = internal resistor determining the current of an internal current stabilizer (typically $14.7 \text{ k}\Omega$ with a spread of +/- 15% correlated to the spread of R_{gasint})

Z_l = load impedance of the line during the measurement

α = gain control factor varying from 1 at $I_{line} = 15 \text{ mA}$ to 0.47 at $I_{line} = 70 \text{ mA}$ when AGC function is applied (see chapter 3.1.4 for details)

Using these typical values in the equation and assuming $Z_{line} = 600 \Omega$, we find a gain equal to:

$$G_v(\text{txaux-ln}) = 20 \times \log A_{vtxa} = 12.6 \text{ dB at } I_{line} = 15 \text{ mA}$$

The input of the TXAUX auxiliary amplifier is biased at two V_d and can handle signals up to 1 Vrms with less than 2% THD and signals up to 50 mVrms with less than 0.1 % THD. Fig. 28 shows the distortion on line versus the rms input signal at $I_{line} = 70 \text{ mA}$.

**TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer**

Application Note

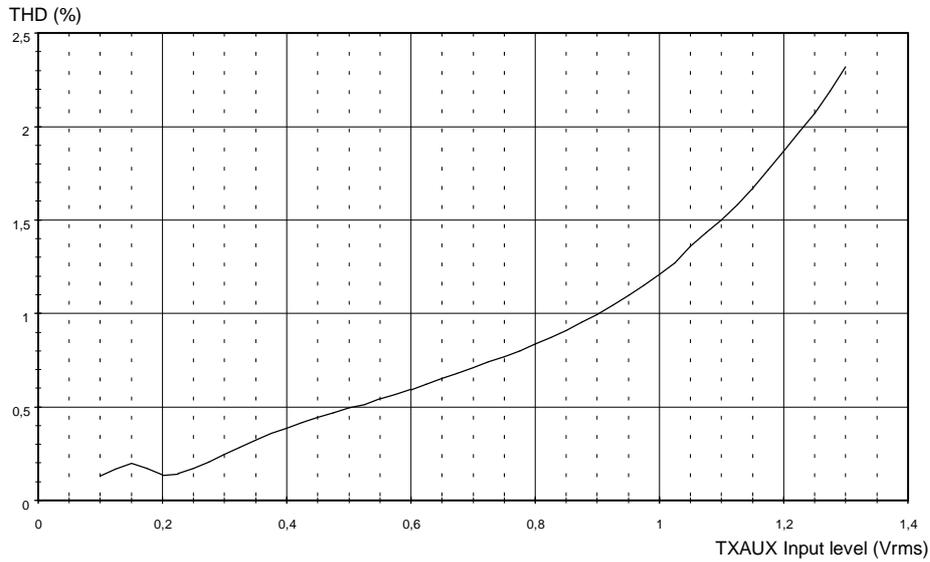


Fig. 28 Distortion on line versus TXAUX input signal

Fig. 29 shows the transmit noise (psophometrically weighted: P53 curve) versus line current when a 2 kΩ resistor is connected between the inputs TXAUX and GND.

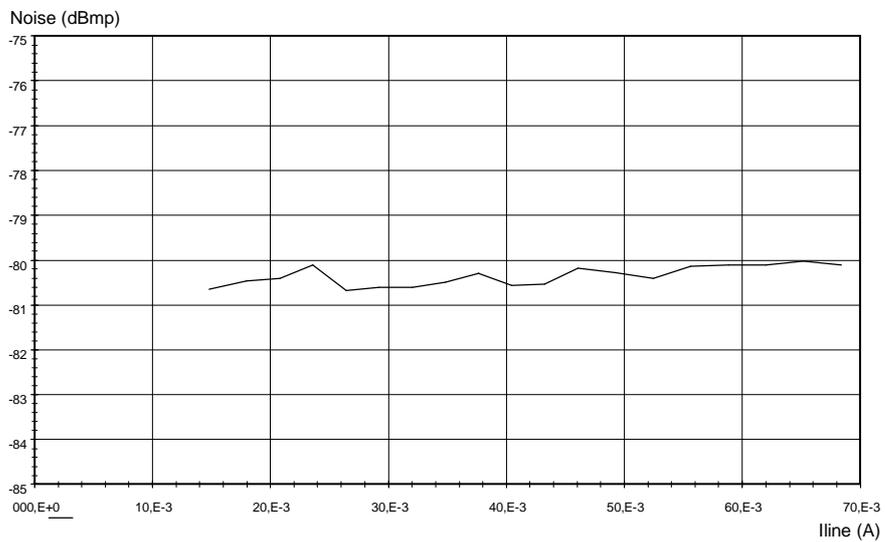


Fig. 29 Transmit noise versus line current

TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer

Application Note

3.4 Receive

The receive part includes four different amplifier outputs: line receive amplifier RECO, earphone amplifier QR, loudspeaker amplifier LSAO, auxiliary receive amplifier AUXO and two different inputs: IR from line and RAUX from auxiliary. The selection of the receive signal is made according to the table of fig. 3.

Fig. 30 shows the block diagram of the receive part while fig. 31 shows the block diagram related to the auxiliary output AUXO.

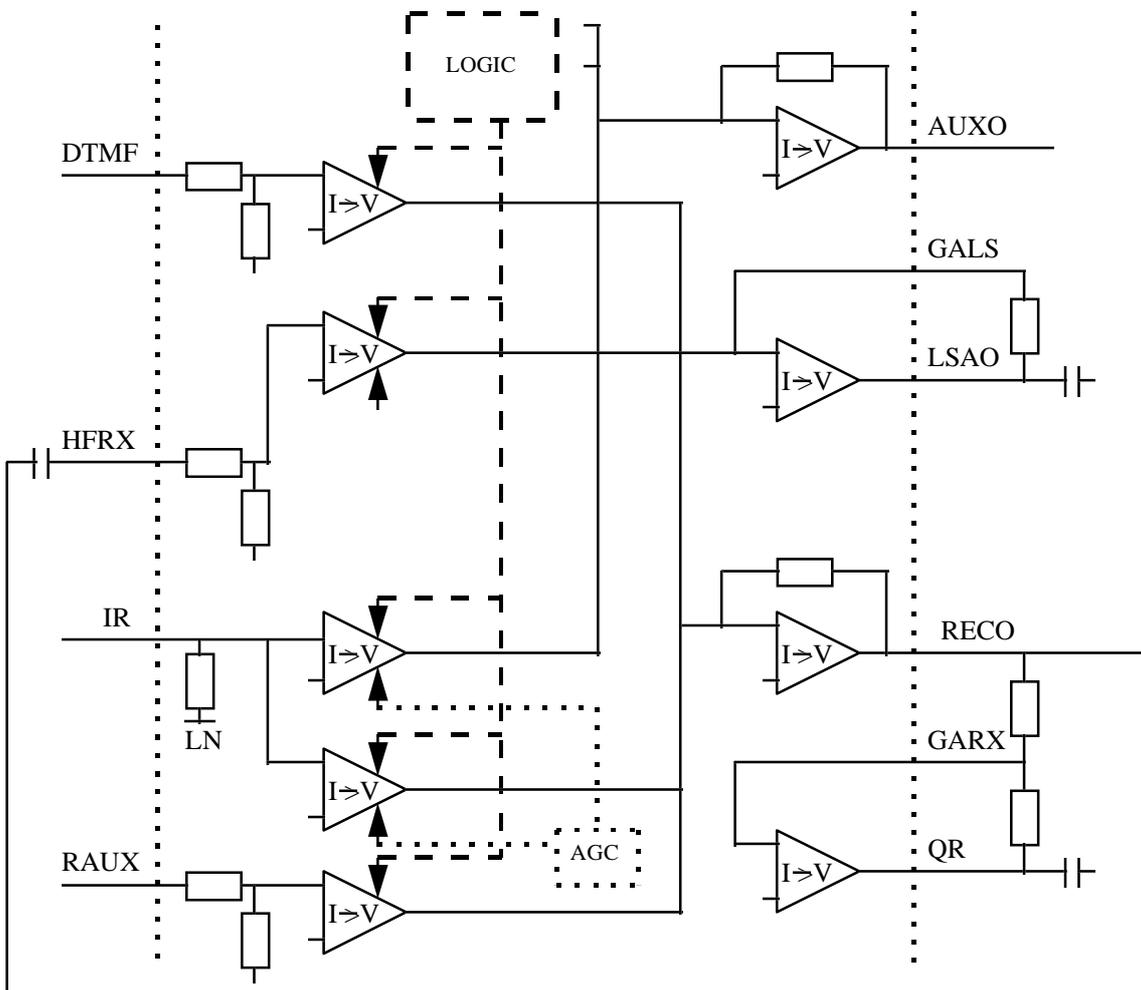


Fig. 30 Receive block diagram

TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer

Application Note

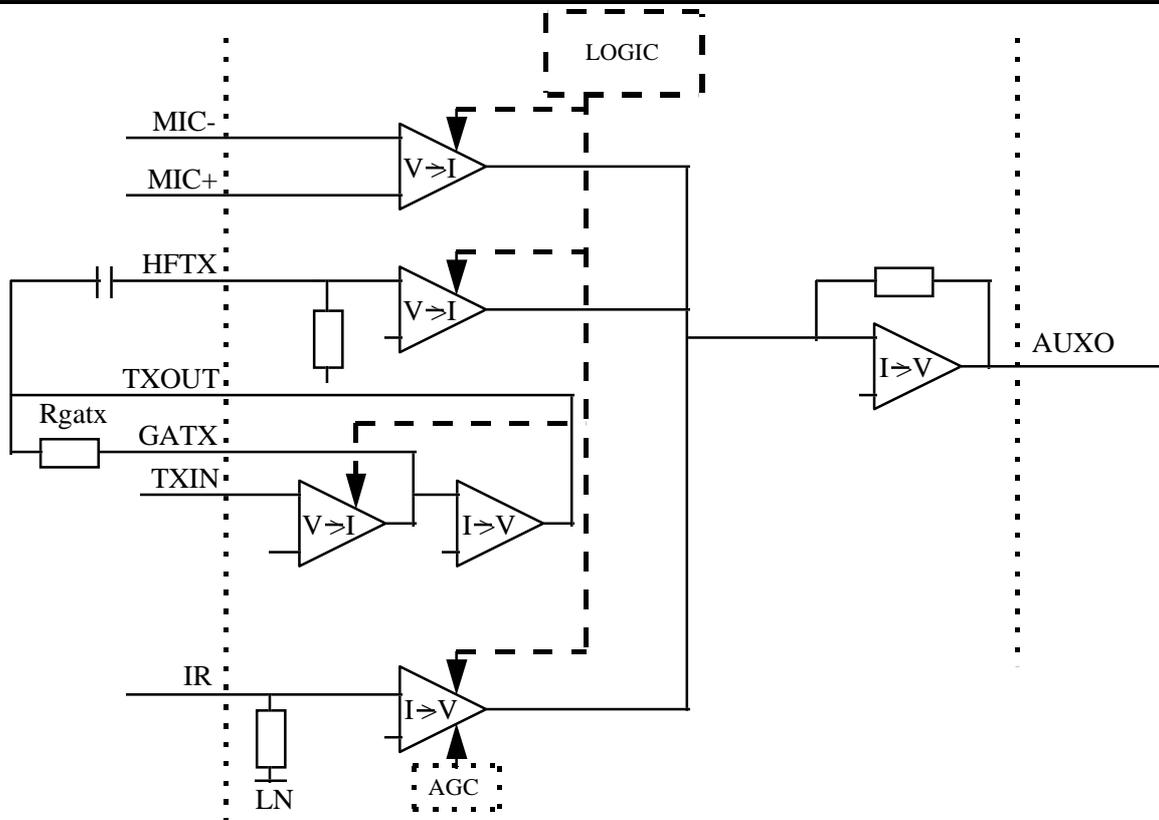


Fig. 31 Block diagram related to AUXO

3.4.1 Line receive amplifier RECO

Principle of operation

According to the logic selection (see fig. 3), the line receive amplifier can get signal from three different inputs: IR for line signals, DTMF for confidence tone and RAUX as auxiliary input.

As can be seen from fig. 30, the line receive amplifier itself is built up out of four parts: three preamplifiers (inputs IR, DTMF and RAUX) which realize a voltage to current conversion and an end-amplifier which realizes the current to voltage conversion.

The RECO output of the TEA1097 has an internal impedance of 125 Ω and is able to drive loads down to an impedance of 5 kΩ.

IR has an a-symmetrical high input impedance between pins IR and LN. It is equal to 20 kΩ with a maximum tolerance of +/-15%. The overall gain $G_v(ir-reco)$ of the receive amplifier from input IR to output RECO is given by the equation:

$$G_v(ir-reco) = 20 \times \log Avrx$$

$$Avrx = 3.5 \times Rgarint/Rrefint \times \alpha$$

with:

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

R_{garint} = internal resistor realizing the current to voltage conversion (typically 128 k Ω with a spread of +/-15%)

R_{refint} = internal resistor determining the current of an internal current stabilizer (typically 14.7 k Ω with a spread of +/- 15% correlated to the spread of R_{garint})

α = gain control factor varying from 1 at $I_{line} = 15$ mA to 0.49 at $I_{line} = 70$ mA when AGC function is applied (see chapter 3.1.4 for details)

Using these typical values in the equation, we find a gain equal to:

$$Gv(ir-reco) = 20 \times \log Avrx = 29.7 \text{ dB} \quad \text{at } I_{line} = 15 \text{ mA}$$

DTMF has an a-symmetrical high input impedance between pins DTMF and GND shared with the DTMF amplifier. It is equal to 20 k Ω with a maximum tolerance of +/-15%. The overall gain $Gv(dtmf-reco)$ of the receive amplifier from input DTMF to output RECO is given by the equation:

$$Gv(dtmf-reco) = 20 \times \log Avmfe$$

$$Avmfe = 0.017 \times R_{garint}/R_{refint}$$

This gain is not affected by the AGC, using these typical values in the equation, we find a gain equal to:

$$Gv(dtmf-reco) = 20 \times \log Avmfe = -16.5 \text{ dB} \quad \text{at } I_{line} = 15 \text{ mA}$$

RAUX has an a-symmetrical high input impedance between pins RAUX and GND. It is equal to 20 k Ω with a maximum tolerance of +/-15%. The overall gain $Gv(raux-reco)$ of the receive amplifier from input RAUX to output RECO is given by the equation:

$$Gv(raux-reco) = 20 \times \log Avrrax$$

$$Avrrax = 0.088 \times R_{garint}/R_{refint}$$

This gain is not affected by the AGC, using these typical values in the equation, we find a gain equal to:

$$Gv(raux-reco) = 20 \times \log Avrrax = -2.3 \text{ dB} \quad \text{at } I_{line} = 15 \text{ mA}$$

Adjustments and performances

29.7 dB of receive gain between IR and RECO compensate approximately the attenuation provided by the antisidetone network minus 2 dB.

Fig. 32 shows the frequency response of the line receive amplifier from IR to RECO at different temperatures.

**TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer**

Application Note

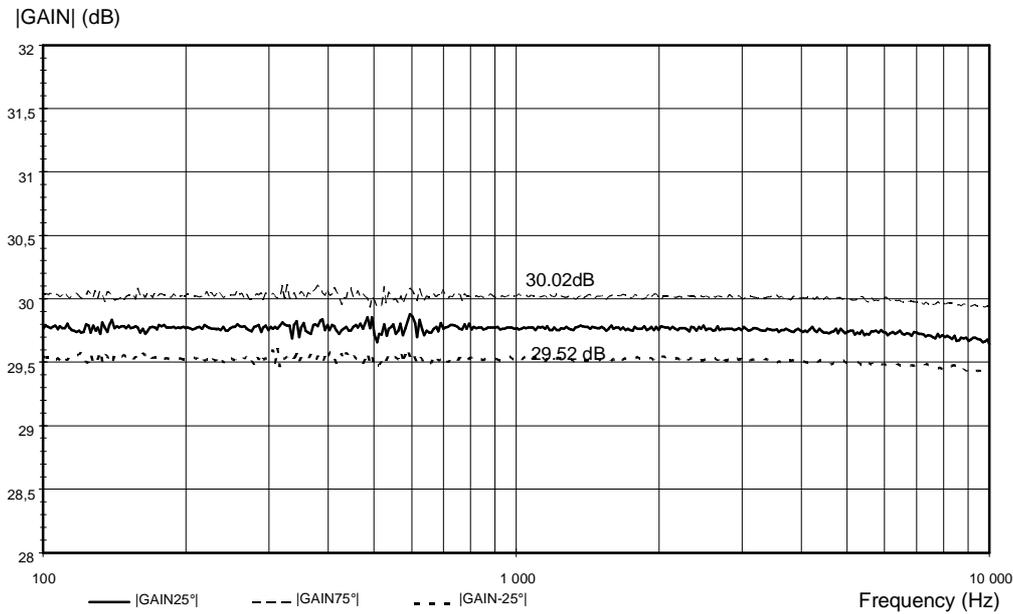


Fig. 32 Receive gain versus frequency: influence of temperature

The output is biased at $2 V_d$ with a temperature drift of $-4 \text{ mV}/^\circ\text{C}$, so the maximum output swing on RECO depends hardly on the value of V_{BB} .

The receive input IR can handle signals up to $50 \text{ mV}_{\text{rms}}$ with less than 2% THD. Fig. 33 shows the distortion on RECO when the limitation is related to the input voltage at IR for a line current equal to 70 mA .

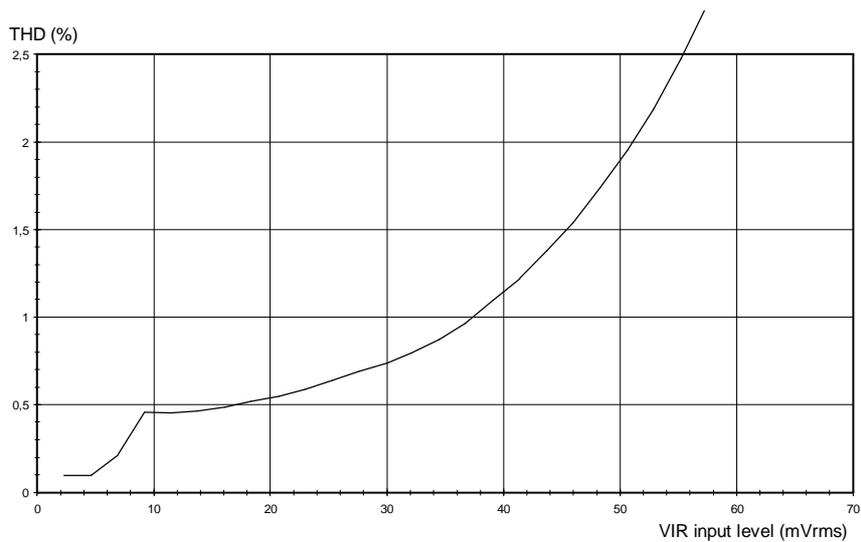


Fig. 33 Distortion on RECO versus input signal on IR

**TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer**

Application Note

The receive input RAUX is biased at 2 Vd and can handle signals up to 900 mVrms with less than 2% THD. Fig. 34 shows the distortion on RECO when the limitation is related to the input voltage at RAUX for a line current equal to 15 mA.

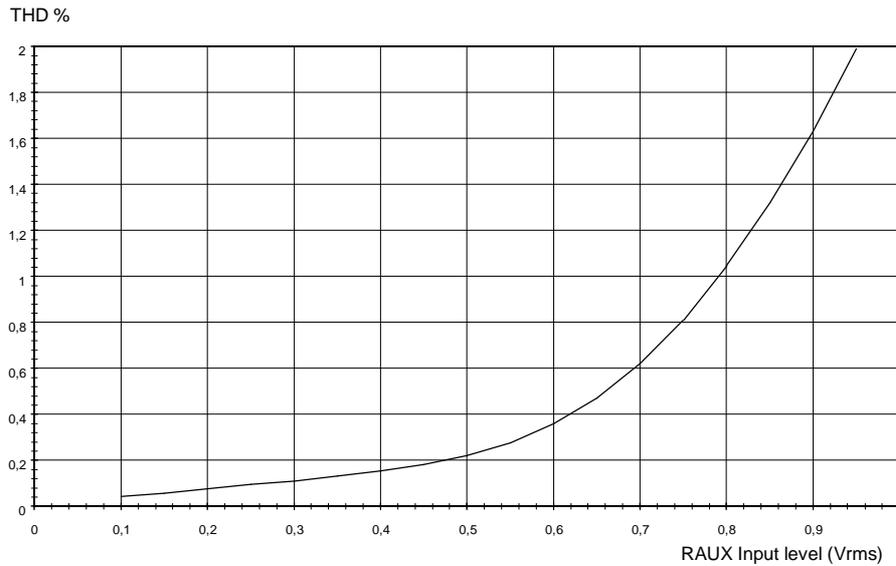


Fig. 34 Distortion on RECO versus input signal on RAUX

Fig. 35 shows the distortion of the signal on RECO as a function of the rms signal on RECO with a load of 5 kΩ and a line current of 15 mA.

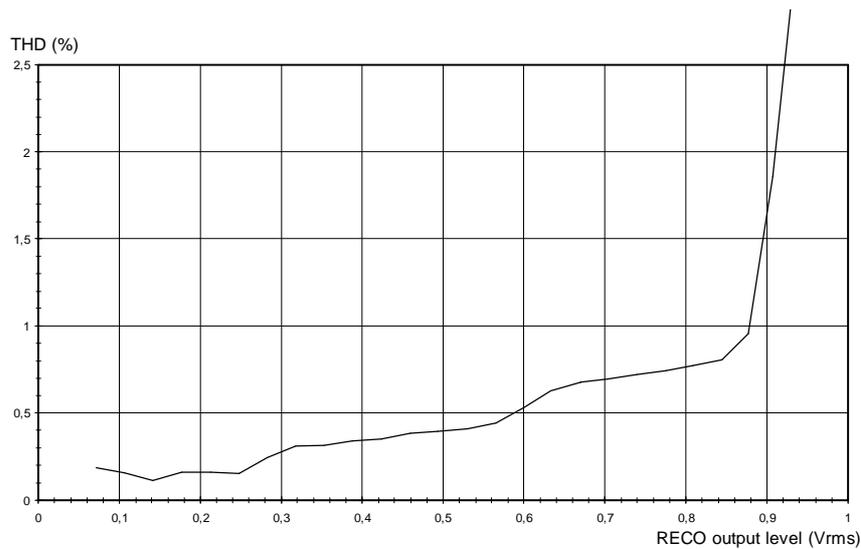


Fig. 35 Distortion on RECO versus level with 5 kΩ load

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

Fig. 36 shows the noise on RECO loaded with 5 k Ω (psophometrically weighted: P53 curve) as a function of the line current. This curve has been done with selection of the input IR which is left open. With the antisidetone network connected to the input IR, part of the microphone noise generated on the line will be added, but thanks to the low microphone noise value, the effect is almost negligible.

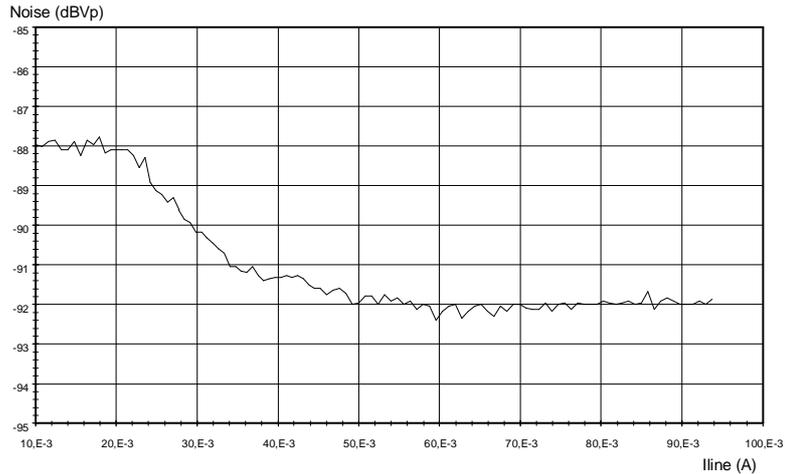


Fig. 36 Noise on RECO

3.4.2 Earphone amplifier QR

Principle of operation

The earphone amplifier of the TEA1097 is able to drive loads down to an impedance of 150 Ω . As can be seen from fig. 30, the earphone amplifier is an amplifier with the gain externally adjustable with a bridge between RECO, GARX and QR. The output is a rail to rail structure suitable for several kind of earpieces and can drive either dynamic, magnetic or piezo-electric earpieces. In case of magnetic or dynamic earpieces, a capacitor in series is required for decoupling; in case of pure capacitive load, a resistor in series is required for stability.

Adjustments and performances

It is possible with a capacitor in series between RECO and GARX to build a high-pass filter and with the capacitor Cgar in parallel with Rgarx to build a low-pass filter. To ensure stability, a capacitor Cgars (Cgars = 10 \times Cgar) between pins GARX and GND is necessary. The output is biased at 2 Vd with a temperature drift of -4 mV/ $^{\circ}$ C, so the value of VBB affects hardly the output swing capability. When the output is not enabled, there is still an AC path through the gain resistors, its attenuation depends on the value of these resistors (a value of 100 k Ω min is advised for one of the resistors). Fig. 37 shows the distortion on QR versus level at Iline = 15 mA on 150 Ω and 470 Ω loads in line powered conditions.

**TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer**

Application Note

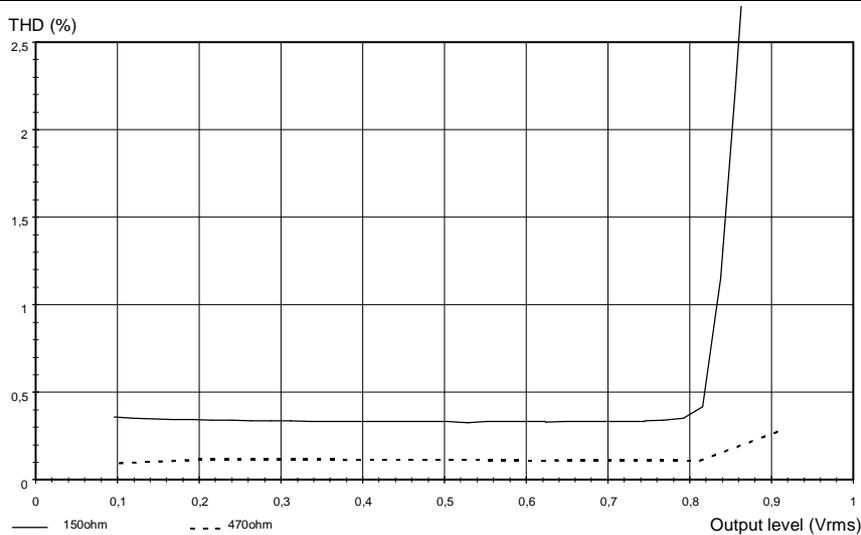


Fig. 37 Distortion on QR versus level

3.4.3 Loudspeaker amplifier LSAO

Principle of operation

As can be seen in fig. 30, the input of the receive channel, pin HFRX is a-symmetrical and the signal has to be referenced to GND. The input HFRX is connected, via a decoupling capacitor, to the receive output RECO. In ring mode, the melody signal is directly connected to pin HFRX via a decoupling capacitor. The output of the loudspeaker amplifier is pin LSAO.

As can be seen in fig. 30, the channel to the loudspeaker amplifier is built up out of two parts: a preamplifier and an end-amplifier. The gain of the preamplifier is determined by the volume control block. The gain of the end-amplifier is determined by the external feedback resistor Rgals.

The overall gain Gvlsao of the loudspeaker amplifier channel from input HFRX to output LSAO is given as:

$$Gvlsao = 20 \times \log Avls$$

$$Avls = 0.35 \times Rgals / Rstab$$

This gain is not affected by the AGC, using these typical values in the equation, we find a gain equal to:

$$Gvlsao = 20 \times \log Avls = 27.8 \text{ dB} \quad \text{when } Rgals = 255 \text{ k}\Omega$$

With Rstab being the resistor at STAB of 3.65 kΩ.

Via the volume control input VOL, the volume of the receive signal can be adjusted by the external potentiometer connected to pin VOL. By increasing the potentiometer resistance, the gain of the preamplifier decreases.

The loudspeaker amplifier is enabled only when VBB becomes higher than 2.9 V; when it is “on” it can be automatically disabled if VBB falls down below 2.7 V but this should not happen in normal line conditions because of the dynamic limiter (see §3.2.1).

A ringer mode is available where only the channel from HFRX to LSAO is enabled; this mode can be used with a Switch Mode Power Supply converting the ringing signal into a DC supply applied at pin ESI. In this mode, a

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

square wave melody signal has to be applied at pin HFRX with an advised amplitude of 200 mVpp (lower than 500 mVpp). The volume control is not operating in this mode.

Adjustments and performances

The input signal for the loudspeaker channel has to be coupled via a decoupling capacitor. Together with the input impedance of 20 k Ω at HFRX, a first order high-pass filter is introduced which can be used to adjust the receive curve and/or to reduce any low frequency unwanted signal coming from the line.

The input HFRX is biased at 2 Vd and can handle signal up to 580 mVrms with a total harmonic distortion of 2%.

The output LSAO must be connected to the loudspeaker via a decoupling capacitor. The output is biased slightly below VBB/2 referenced to GND in order to optimize the output power, even with an 8 Ω loudspeaker. With the resistor Rgals, the gain of the loudspeaker amplifier channel can be adjusted from 0 to +35 dB. The gain equals typically 27.8 dB with resistor Rgals = 255 k Ω . A capacitor Cgals can be connected in parallel with Rgals to provide a low-pass filter which can be used to adjust the loudspeaker amplifier curve. A capacitor Cgals of at least 150 pF is recommended in ringer mode.

The output drive capability at pin LSAO is typically 300 mApeak.

The noise level at the output LSAO is -79 dBVp at a gain of 28 dB and with the input HFRX left open.

Out of pin VOL a current Ivol, set by Rstab, is flowing which is proportional to the absolute temperature (PTAT). At room temperature this current is around 5 μ A. Together with the resistance of the potentiometer, the current Ivol creates a PTAT voltage on pin VOL. This PTAT voltage is processed by the volume control block; as a result, a temperature independent volume reduction of the output receive signal of 3 dB is obtained at approximately every increase of 1900 Ω of the potentiometer resistance.

This means that a linear potentiometer can be used to control the volume logarithmically, thus in dB. With the advised value of 22 k Ω , the maximum gain reduction of the volume control is more than 30 dB.

When digital volume control is desired, the switches can be either MOSFETs or analog switches with very low DC and AC resistance. Due to saturation voltage, it is advised not to use bipolar transistors as switches.

In line powered condition, matching between operating current range and impedance of loudspeaker is important (below approximately 27 mA, a 32 Ω loudspeaker provides more power than a 25 Ω one), Fig. 16 shows the output level on LSAO versus line current on 16 Ω and 50 Ω loads in series with 220 μ F in handsfree mode and nominal line powered conditions.

When an external power supply is connected at pin ESI, the LSAO can drive loudspeakers with an impedance down to 8 Ω .

Fig. 38 shows the output power in ringer mode versus the input current at ESI.

**TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer**

Application Note

Plsao for 2% thd on Isao
(Vrms)

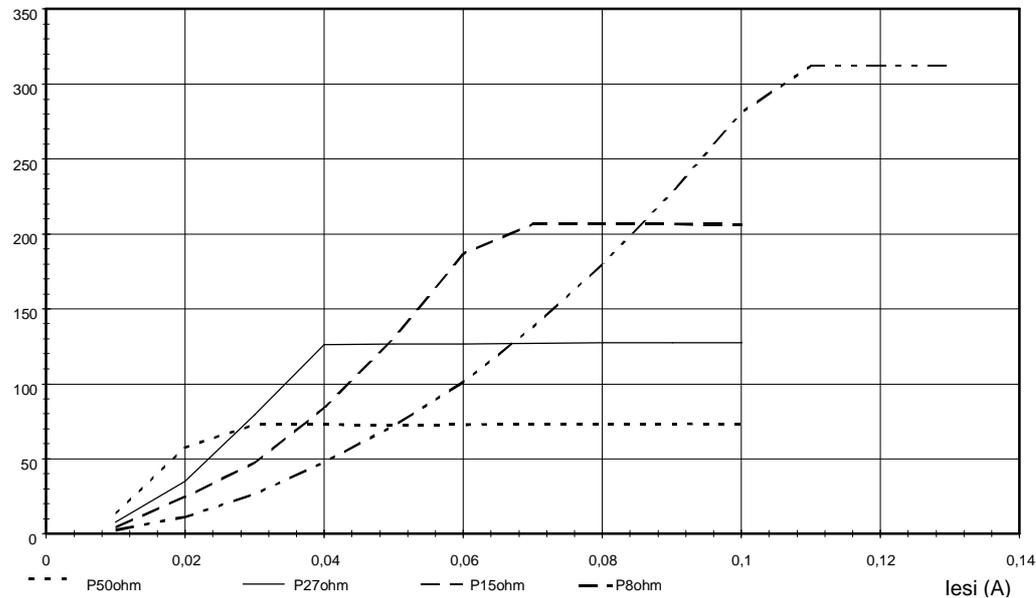


Fig. 38 Output level in ring mode versus input current at ESI

3.4.4 Auxiliary receive amplifier AUXO

Principle of operation

According to the logic selection (see fig. 3), the auxiliary receive amplifier can get signal from three different inputs: IR for line signals, HFTX from TXOUT (e.g. intercom or answering machine applications) and MIC+/MIC- (e.g. intercom or answering machine applications).

As can be seen from fig. 31, the auxiliary receive amplifier itself is built up out of four parts: three preamplifiers (inputs IR, HFTX and MIC+/MIC-) which realize a voltage to current conversion and an end-amplifier which realizes the current to voltage conversion.

The AUXO output of the TEA1097 has an internal impedance of 125 Ω and is able to drive loads down to an impedance of 5 kΩ.

IR has an a-symmetrical high input impedance between pins IR and LN shared with the IR to RECO amplifier. It is equal to 20 kΩ with a maximum tolerance of +/-15%. The overall gain Gv(ir-auxo) of the auxiliary receive amplifier from input IR to output AUXO is given by the equation:

$$Gv(ir-auxo) = 20 \times \log Avrax$$

$$Avrax = 6.66 \times Rgara/Rrefint \times \alpha$$

with:

Rgara = internal resistor realizing the current to voltage conversion (typically 96.3 kΩ with a spread of +/-15%)

Rrefint = internal resistor determining the current of an internal current stabilizer (typically 14.7 kΩ with a spread of +/- 15% correlated to the spread of Rgara)

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

α = gain control factor varying from 1 at $I_{line} = 15$ mA to 0.49 at $I_{line} = 70$ mA when AGC function is applied (see chapter 3.1.4 for details)

Using these typical values in the equation, we find a gain equal to:

$$Gv(ir-auxo) = 20 \times \log Avrax = 32.8 \text{ dB at } I_{line} = 15 \text{ mA}$$

HFTX has an a-symmetrical high input impedance between pins HFTX and GND. It is equal to 20 k Ω with a maximum tolerance of +/-15% and the input is biased at 2 Vd. The overall gain $Gv(hftx-auxo)$ of the auxiliary amplifier from input HFTX to output AUXO is given by the equation:

$$Gv(hftx-auxo) = 20 \times \log Avbmax$$

$$Avbmax = 0.88 \times Rgara/Rrefint$$

This gain is not affected by the AGC, using these typical values in the equation, we find a gain equal to:

$$Gv(hftx-auxo) = 20 \times \log Avbmax = 15.2 \text{ dB}$$

MIC+/MIC- has symmetrical high input impedances (typically 70 k Ω -2 times 35 k Ω - between pins MIC+ and MIC- with maximum tolerances of +/- 15%) shared with the MIC+/MIC- to LN amplifier. It is equal to 20 k Ω with a maximum tolerance of +/-15%. The overall gain $Gv(mic-auxo)$ of the auxiliary handset microphone amplifier from input MIC+/MIC- to output AUXO is given by the equation:

$$Gv(mic-auxo) = 20 \times \log Avhmax$$

$$Avhmax = 2.78 \times Rgara/Rrefint$$

This gain is not affected by the AGC, using these typical values in the equation, we find a gain equal to:

$$Gv(mic-auxo) = 20 \times \log Avhmax = 25.2 \text{ dB}$$

Adjustments and performances

32.8 dB of receive gain between IR and AUXO compensate approximately the attenuation provided by the antisidetone network.

Fig. 39 shows the frequency response of the auxiliary receive amplifier from IR to AUXO at different temperatures.

**TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer**

Application Note

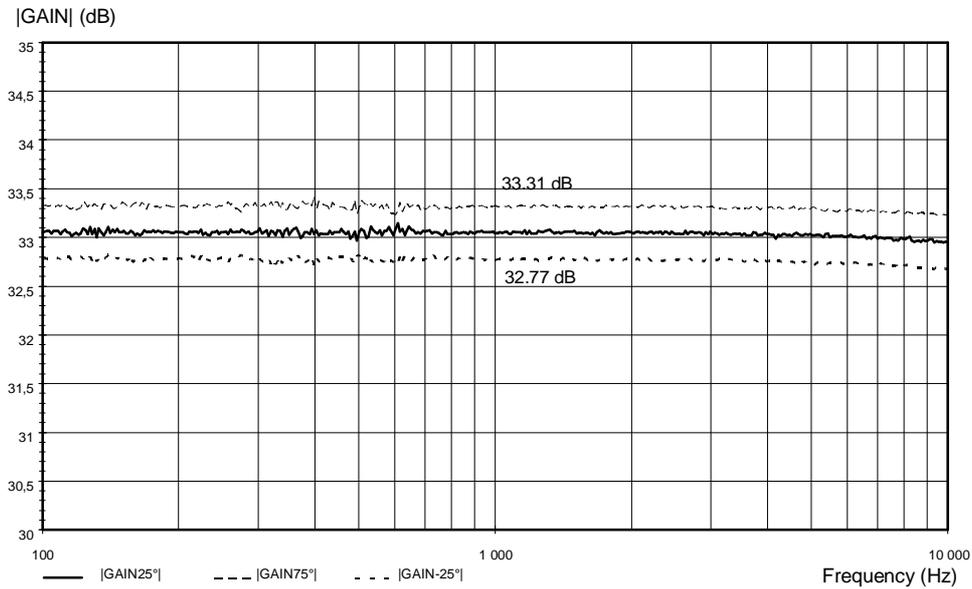


Fig. 39 Auxiliary receive gain versus frequency, influence of temperature

The output is biased at 2 Vd with a temperature drift of -4 mV/°C, so the maximum output swing on AUXO depends hardly on the value of VBB.

The receiving input IR can handle signals up to 50 mVrms with less than 2% THD. Fig. 40 shows the distortion on AUXO for a line current equal to 75 mA.

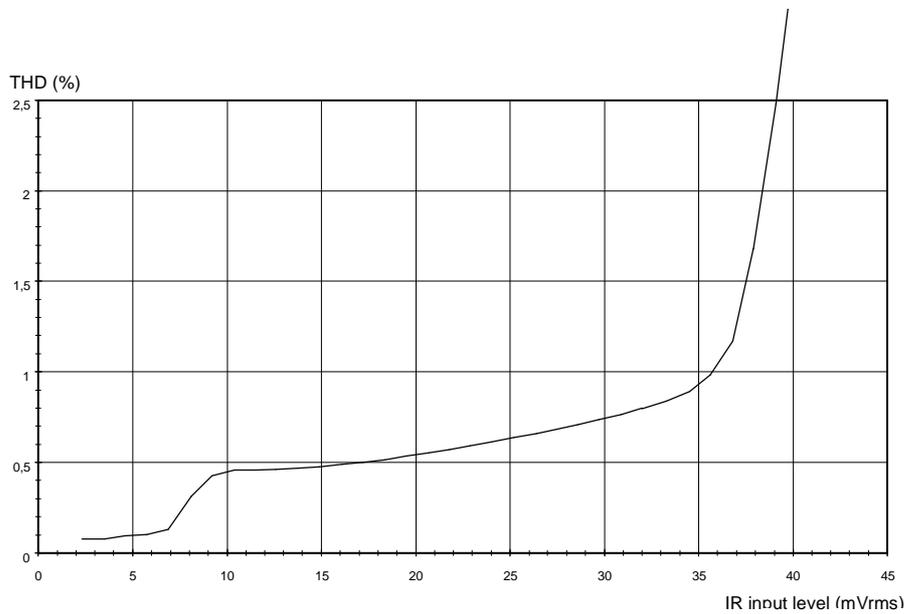


Fig. 40 Distortion on AUXO versus input signal on IR

The input HFTX is biased at 2 Vd and can handle signals up to 140 mVrms with less than 2% THD. Fig. 41 shows the distortion on AUXO for a line current equal to 75 mA.

**TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer**

Application Note

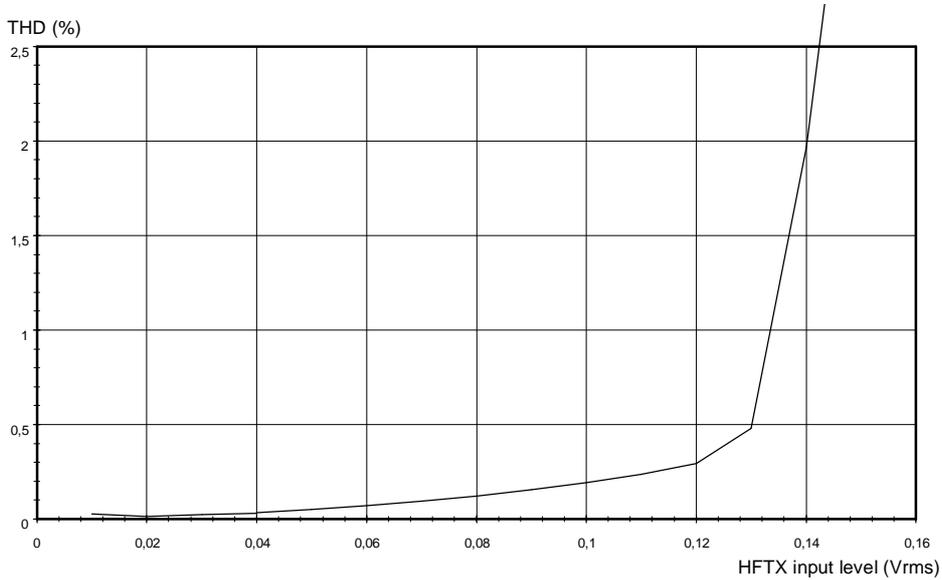


Fig. 41 Distortion on AUXO versus input signal on HFTX

Fig. 42 shows the distortion of the signal on AUXO as a function of the rms signal on AUXO with a load of 5 kΩ and a line current of 15 mA.

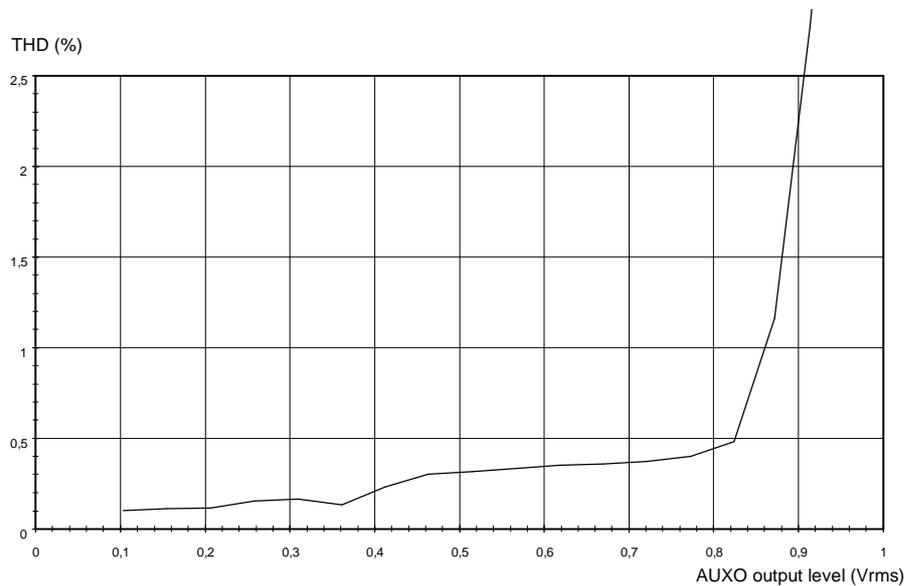


Fig. 42 Distortion on AUXO versus level with 5 kΩ load

Fig. 43 shows the noise on AUXO loaded with 5 kΩ (psophometrically weighted: P53 curve) as a function of the line current. This curve has been done with selection of the input IR which is left open. With the antisidetone network connected to the input IR, part of the microphone noise generated on the line will be added but, thanks to the low microphone noise value, the effect is almost negligible. Fig. 44 shows the noise on AUXO when the input is from MIC+/MIC-.

**TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer**

Application Note

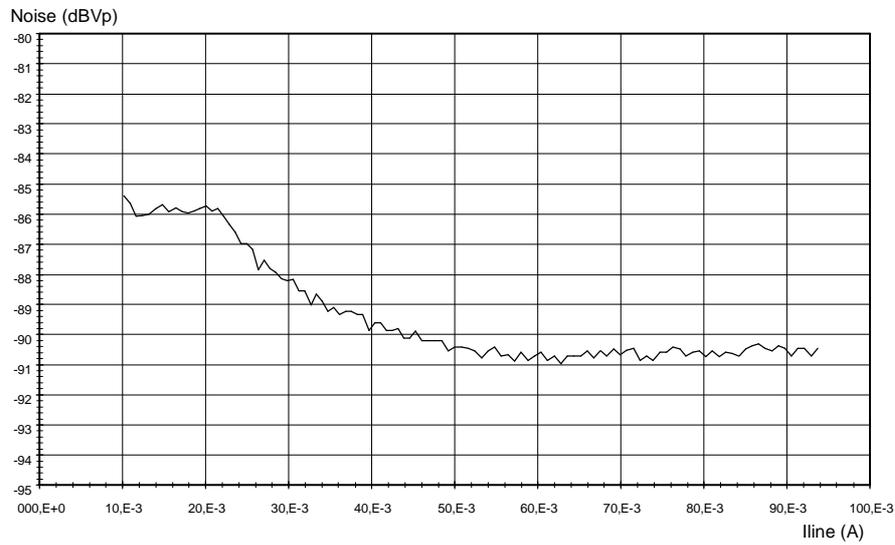


Fig. 43 Noise on AUXO with input at IR

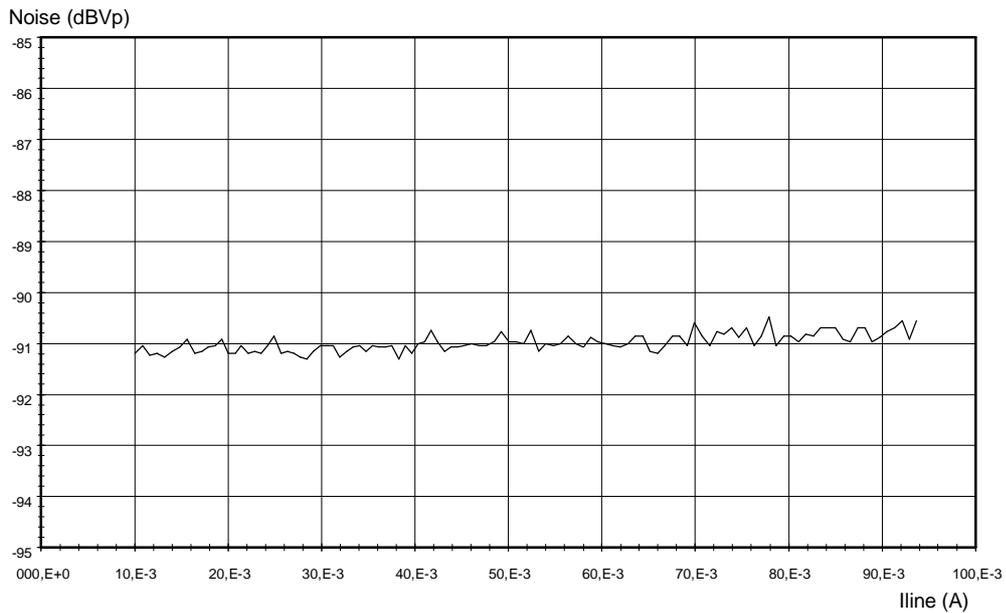


Fig. 44 Noise on AUXO with input at MIC+/MIC-

3.4.5 Auxiliary microphone monitor amplifier

When Group-listening mode is selected, the microphone signal is monitored with a fixed gain of 49.8 dB and a spread of +/- 2.5 dB at the output TXOUT. In this condition, the end-amplifier of the base microphone channel is switched into high impedance output mode. The channel between MIC+/MIC- and TXOUT is built up out of two parts: a preamplifier which makes a voltage to current conversion followed by an end-amplifier which realizes the current to voltage conversion.

**TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer**

Application Note

The output is biased at $2 V_d$ and can drive up to $\pm 300 \mu A$ rms and the maximum output swing is $V_{BB}-0.8V$.

An external antihowling circuit is shown in §5 fig. 54 while the block diagram of the Group-listening application is shown fig. 49.

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

Miscellaneous

Ground layout

The layout of the ground is very important for noise and digital handsfree applications. In fact, high currents generate residual voltages on the PCB and these voltages may affect dramatically some references or may couple loudspeaker signal with microphone. Fig. 45 gives a reference for the connection of different components to the grounds.

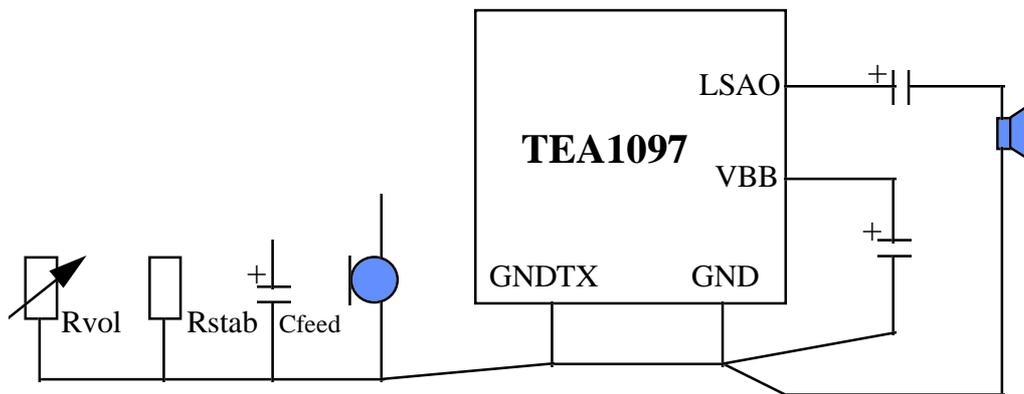


Fig. 45 GND and GNDTX connections

Antihowling

In group-listening application there is an acoustic coupling between the loudspeaker and the handset microphone. When the microphone is too close to the loudspeaker, the gain of the loop becomes higher than 1 and howling occurs. This howling may disturb the other party, specially if it is an operator with a headset. Around the TEA1097 it is possible to build an antihowling circuit which limits this howling. For this purpose, in group-listening mode, the microphone signal is amplified by 49.8 dB at pin TXOUT and the gain of the loudspeaker amplifier can be reduced by pulling pin DLC to GND. The solution advised for this antihowling circuit is to measure the amplitude of the signal at pin TXOUT, when it is too high for a too long time pull the pin DLC to GND. This can be done with a very simple circuit where the time constants are set by capacitors (see fig. 54).

Ringer mode

In the ringer mode provided, a switch mode power supply circuit (DC/DC converter) has to be added to convert the input ringing signal into a DC supply connected at pin ESI. The current coming from this supply is usually varying with the frequency of the input signal thus modulating the melody with this low frequency. It is possible to reduce the acoustic effect of this modulation by slowing down the dynamic limiter. This can be done by increasing the value of Cdlc in ringer mode from 0.47 μF to 10 μF (switching a parallel 10 μF capacitor by means of a DMOS transistor).

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

3.5 Logic block

3.5.1 Logic inputs

In this chapter the 5 logic inputs which control the TEA1097 are described. The selected channels for each combination of the logic inputs are depicted in fig. 46. When a channel is selected, the relevant preamplifier is switched-on and all the others connected to the same end-amplifier are switched-off. The end-amplifiers and the electret microphone supply are also enabled or disabled according to fig. 46.

In order to guarantee handset conversation mode when an other set is connected in parallel and when the line current is so low that the dialler or the microcontroller can't operate, the values of the logic inputs are ignored when VBB has not been higher than 2.9 V or has fallen down below 2.5 V and the handset conversation mode is forced (see §3.2.1).

Input PD/

This input is active low, it can be driven by an open drain structure because a pull-up to VBB is included. Nevertheless, in case of I/O structure on the microcontroller side, a push-pull output structure is recommended to polarize properly the input of the microcontroller when VBB varies (no current will flow from VDD to VBB via this pin). The threshold voltage level is 0.65 V typically with a temperature coefficient of -2 mV/°C. The input voltage must stay within the limits GND -0.4 V to VBB +0.4 V.

Except in ring mode (see fig. 46), when PD/ is low all the internal consumptions are switched-off, only the supply block VDD is kept active in order to sink current from the tank capacitor connected at VBB.

Input MUTT/

This input is active low, it can be driven by an open drain structure because a pull-up to VBB is included. Nevertheless, in case of I/O structure on the microcontroller side, a push-pull output structure is recommended to polarize properly the input of the microcontroller when VBB varies (no current will flow from VDD to VBB via this pin). The threshold voltage level is 0.65 V typically with a temperature coefficient of -2 mV/°C. The input voltage must stay within the limits GND -0.4 V to VBB +0.4 V.

Input MUTR/

This input is active low, it must be driven by a push-pull structure, the threshold voltage level is 0.65 V typically with a temperature coefficient of -2 mV/°C. The input voltage must stay within the limits GND -0.4 V to VBB +0.4 V.

Input HFC

This input is active high, it can be driven by an open drain structure because the pull-down is included, the threshold voltage level is 1.3 V typically with a temperature coefficient of -4 mV/°C. The input voltage must stay within the limits GND -0.4 V to VBB +0.4 V.

If the supply conditions are such that the handset conversation mode is forced, this pin becomes an output at logic level "0" with an output sink capability of 300 μ A.

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

Input AUXC

This input is active high, it can be driven by an open drain structure because the pull-down is included, the threshold voltage level is 0.65 V typically with a temperature coefficient of -2 mV/°C. The input voltage must stay within the limits GND -0.4 V to VBB +0.4 V.

3.5.2 Connections

The following table gives the details of the connections which are enabled according to the logic inputs and some ideas of applications which are foreseen.

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

	LOGIC INPUTS					CONNECTIONS	APPLICATIONS
	PD/	HFC	MUTT/	MUTR/	AUXC		
1	0	X	X	X	1	HFRX -> LSAO	Ring mode with SMPS
2	0	X	X	X	0		Flash, DC dialling
3	1	0	0	0	0	DTMF->LN ; CT->RECO (MICS, QR)	Tel. Set: DTMF dialling
4	1	0	0	1	0	MIC->AUXO; RAUX->RECO (MICS, QR)	Cordless intercom with handset; A.M.(record or listen with handset)
5	1	0	0	1	1	MIC->AUXO; RAUX->RECO (QR)	
6	1	0	1	X	0	MIC->LN; IR->RECO; IR->AUXO MIC->TXOUT (MICS, QR)	Handset conversation; A.M. (record conv.)
7	1	0	1	1	1	MIC -> LN; MIC -> TXOUT (QR)	
8	1	0	1	0	1	TXAUX->LN ; IR->AUXO	Conversation with auxiliary (Fax, A.M., RF interface,...); Cordless: digital handsfree in mobile
9	1	0	0	0	1	TXAUX->LN ;IR->AUXO; RAUX ->RECO	
10	1	1	1	1	1	TXIN->TXOUT; TXAUX->LN; IR->RECO	
11	1	1	0	1	1	RAUX->RECO; HFRX->LSAO	Listening on loudspeaker
12	1	1	0	0	1	TXAUX->LN ; IR->AUXO; RAUX->RECO; HFRX->LSAO	Answering Machine (outgoing message)
13	1	1	0	0	0	DTMF->LN ; CT->RECO; HFRX->LSAO (MICS, QR)	HF/GL Tel Set DTMF dialling
14	1	1	1	0	1	TXAUX->LN ; IR->AUXO; IR->RECO; HFRX->LSAO	Answering machine (incoming message); Fax with monitoring
15	1	1	0	1	0	TXIN->TXOUT; HFTX->AUXO; RAUX->RECO; HFRX->LSAO (MICS)	Cordless intercom with base; A.M. (record or listen with base)
16	1	1	1	1	0	TXIN->TXOUT; TXAUX->LN; IR->RECO; IR->AUXO; HFRX->LSAO (MICS)	Digital handsfree conversation; A.M. (record conv.)
17	1	1	1	0	0	MIC->LN; IR->RECO; IR->AUXO; HFRX->LSAO ; MIC->TXOUT (MICS,QR)	Group-listening conversation; A.M. (record conv.)

Fig. 46 Table of connections

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

In modes 1, the volume control doesn't operate.

When VBB has not reached a value higher than 2.9 V or has fallen down below 2.5 V, the logic inputs are ignored and the handset conversation mode is forced:

MIC -> LN

IR -> RECO

MICS, QR are "active"

**TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer**

Application Note

4. APPLICATION COOKBOOK

In this chapter, the procedure for making a line-powered handset plus mains powered digital handsfree application with the TEA1097 is given (see general architecture of fig; 50). With the help of fig. 55 in appendix, the design flow is given as a number of steps which should be made. As far as possible for every step, the components involved and their influence on every step are given.

Fig. 55 is the schematic of the OM5848 demoboard, so the values of the components are proposed but the adaptation to the application can be done by modifying these values.

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

Step	Adjustment
DC setting :	
Adjust the DC setting of the TEA1097 to the local PTT requirements.	
Voltage LN-GND	This voltage can be adjusted by increasing V_{ref} up to 7 V at max line current with the R_{va} resistor between pins REG and SLPE.
DC slope	Not advised to modify.
Supply point VBB	Optimize the value of C_{vbb} .
Supply point VDD	Optimize the value of C_{vdd} .
Artificial inductor	Its value can be adjusted by changing the value of C_{reg} : a smaller value speeds-up the DC current shape during transients but decreases the value of the inductance and therefore affects the BRL at low frequencies.

Impedance, sidetone and AGC :

After setting the required set impedance, the sidetone has to be optimized using the sidetone network in order to minimize the loop gain in all line conditions. AGC can be adjusted at that step.

Set passive impedance	The BRL is adjusted with the impedance network connected between LN and GND ($R_{cc} + R_z // C_z$ in series with C_{cz}).
Sidetone	Adjust Z_{bal} (R_{bal1} , R_{bal2} , C_{bal}) according to the line characteristics.
AGC	Internally defined, the characteristics (I_{start} and I_{stop}) can be shifted to higher line currents with an external R_{agc} resistor connected between AGC and LN. In case it is necessary to shift I_{start} and I_{stop} to lower current values, the value of R_{slpe} may be slightly increased proportionally (see §3.1.4).

TEA1097 transmit and receive gains in handset mode

Handset microphone gain	The microphone gain of the application has to be adjusted before entering pins MIC+/MIC- of the TEA1097. It can be reduced by using the resistor R_{tx3} which forms a bridge attenuator with R_{tx1} and R_{tx2} . C_{tx1} , C_{tx2} form a high-pass filter with R_{tx1} , R_{tx2} in series with the input impedance at MIC+/MIC-. A capacitor C_{mich} forms a low-pass filter with the impedance of the microphone and the resistors R_{micp}/R_{micm} . The gain between MIC+/MIC- and LN is 44.1 dB on 600 Ω .
Receive gain	Receive gain of the handset has to be adjusted with earphone amplifier with the resistor R_{e1} . A capacitor C_{gar} in parallel with R_{e2} forms a low-pass filter. stability is ensured with capacitor C_{gars} ($10 \times C_{gar}$) between pins GARX and VEE. The gain between IR and RECO is fixed at 29.7 dB.

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

Step	Adjustment
TEA1097 transmit gain in digital handsfree mode	
After the sensitivity and the curve of the microphone are adjusted, the gain can be adjusted to the desired value	
Microphone sensitivity	Rbmics sets the sensitivity and provides the polarisation of the electret. Cmicb with Rbmics and the output impedance of the electret form a low-pass filter.
Frequency curve	Ctxin with the 20 kΩ input impedance at TXIN form a high-pass filter.
Transmit gain and stability	Rgatx sets the microphone amplifier gain : $G_v(\text{txin-txout}) = 20 \times \log(0.7 \times R_{\text{gatx}}/R_{\text{stab}})$ The capacitor Catx in parallel with Rgatx forms a low-pass filter. The gain between TXAUX and LN is fixed at 12.6 dB on 600 Ω. Ctxax and TXAUX input impedance of 20 kΩ form a high-pass filter. A resistor bridge attenuator may be inserted between the codec output and TXAUX or between Ctxin and TXIN.
TEA1097 receive channel for digital handsfree	
The gain of the receive pass and the curve can be adjusted. The volume control range can be chosen.	
Receive gain	The gain between IR and AUXO is 32.8 dB which compensate the sidetone attenuation.
Receive curve	Caxo with the input impedance of the codec form a high-pass filter.
TEA1097 loudspeaker amplifier :	
The gain is adjustable with Rgals, a high-pass filter can be made, the dynamic limiter timing can be chosen.	
Gain and frequency curve	Rgals sets the loudspeaker amplifier gain : $G_v(\text{lsao}) = 20 \times \log(0.35 \times R_{\text{gals}}/R_{\text{stab}})$ Cgals forms a low-pass filter with Rgals. Chrx and Clso in series with loudspeaker can form high-pass filters.
Dynamic limiter timing	Capacitor Cdlc at pin DLC
Volume control	A linear potentiometer of 22 kΩ is suggested (3 dB for each 1.9 kΩ).

Fig. 47 Steps in the design flow of the TEA1097

**TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer**

Application Note

5. APPLICATION EXAMPLES

In this chapter, some general block diagrams are provided to show the integration method of the TEA1097 in different terminal applications.

Moreover, a demoboard (OM5848) is available. As the TEA1097 may be used in various applications, this demoboard includes only the TEA1097 with its basic environment. Its schematic is shown in fig. 55 while its component placement diagram is in fig. 56.

On this schematic, the components which are connected with dotted lines are for RFI immunity purpose only. Moreover, a proposal of external antihowling circuitry is included on the layout of the PCB (its components are not equipped) with its input at TXOUT and output on DLC.

TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer

Application Note

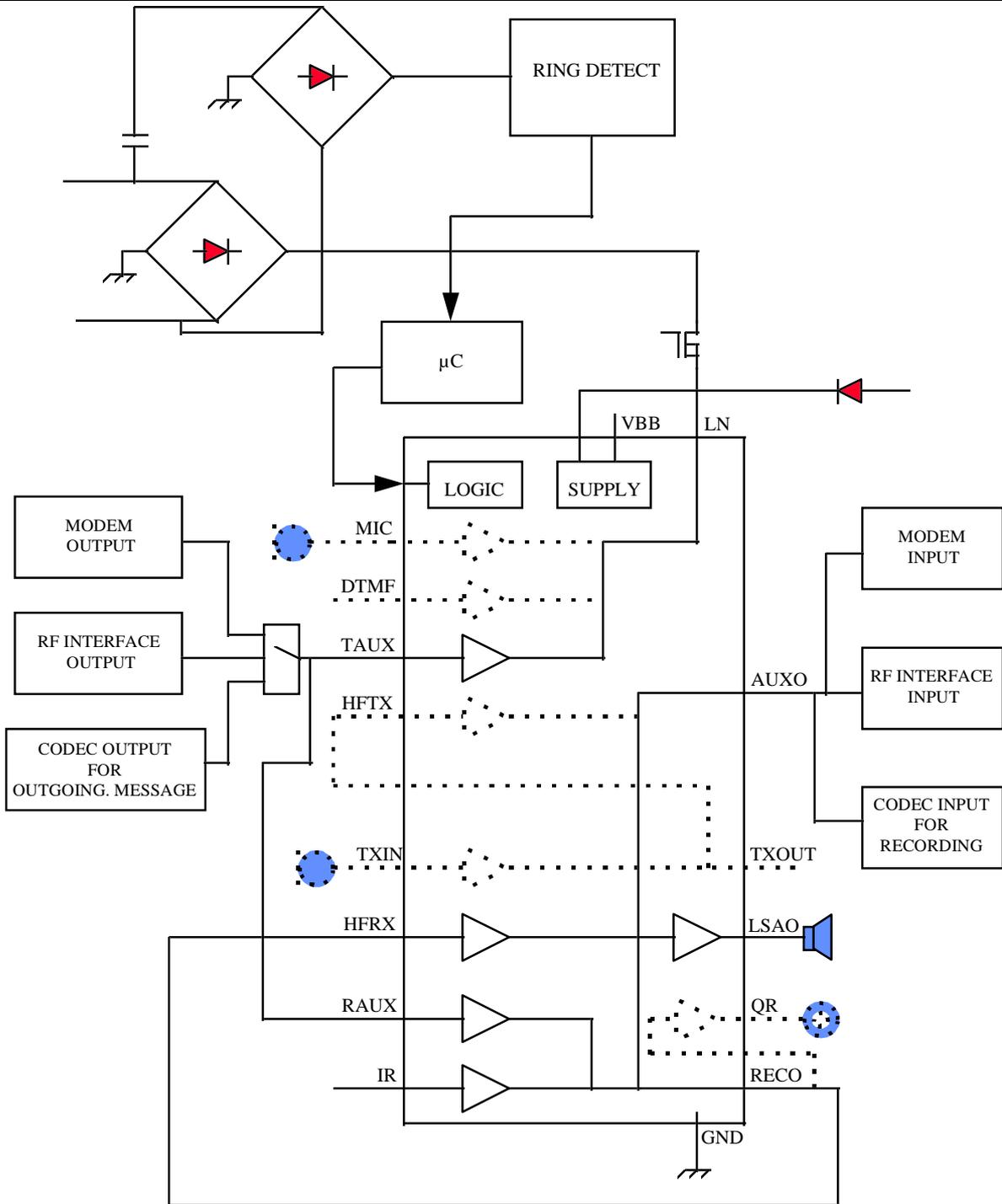


Fig. 48 Telephone-Answering Machine + Cordless + Fax connections

TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer

Application Note

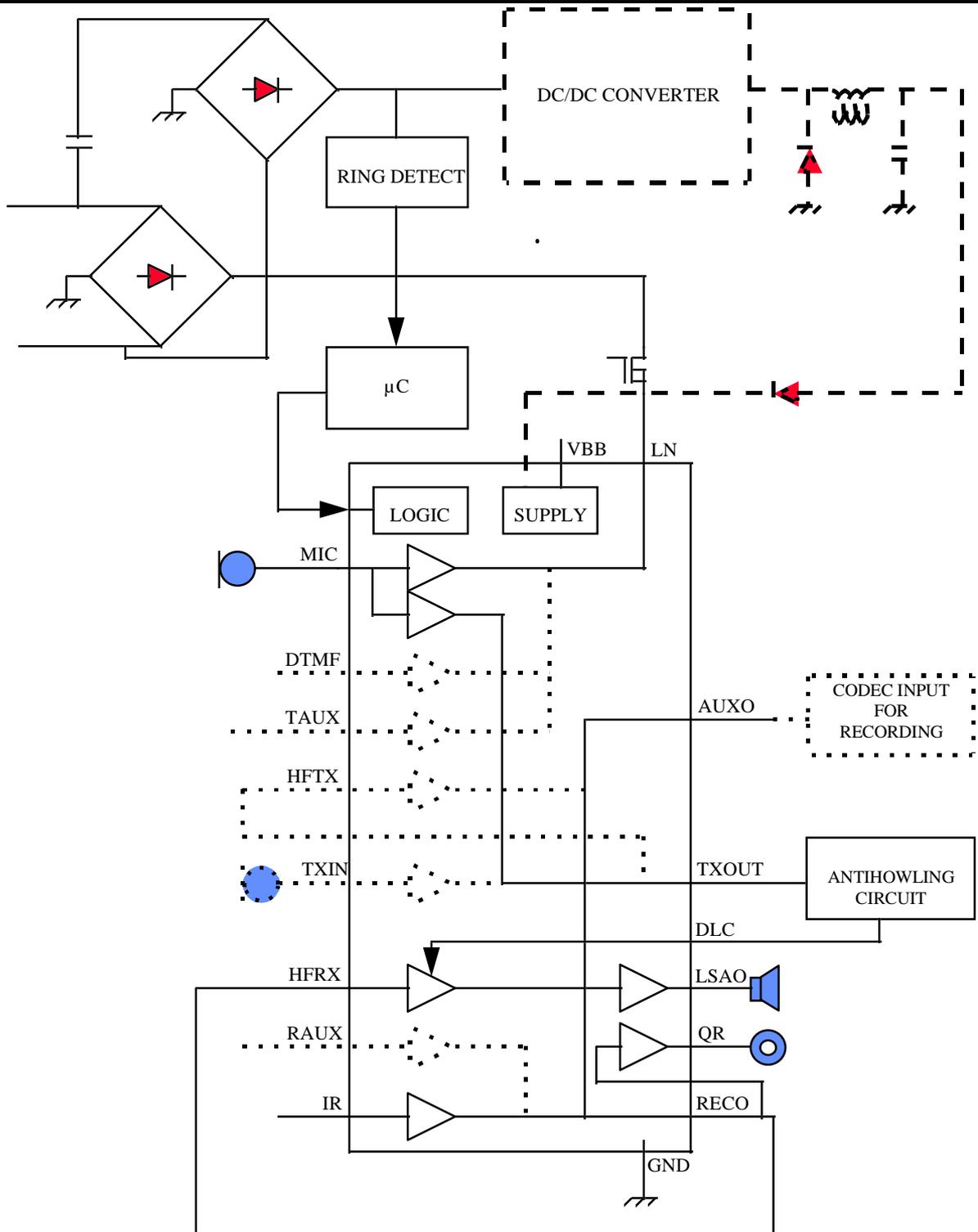


Fig. 49 Group-listening conversation with antihowling

TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer

Application Note

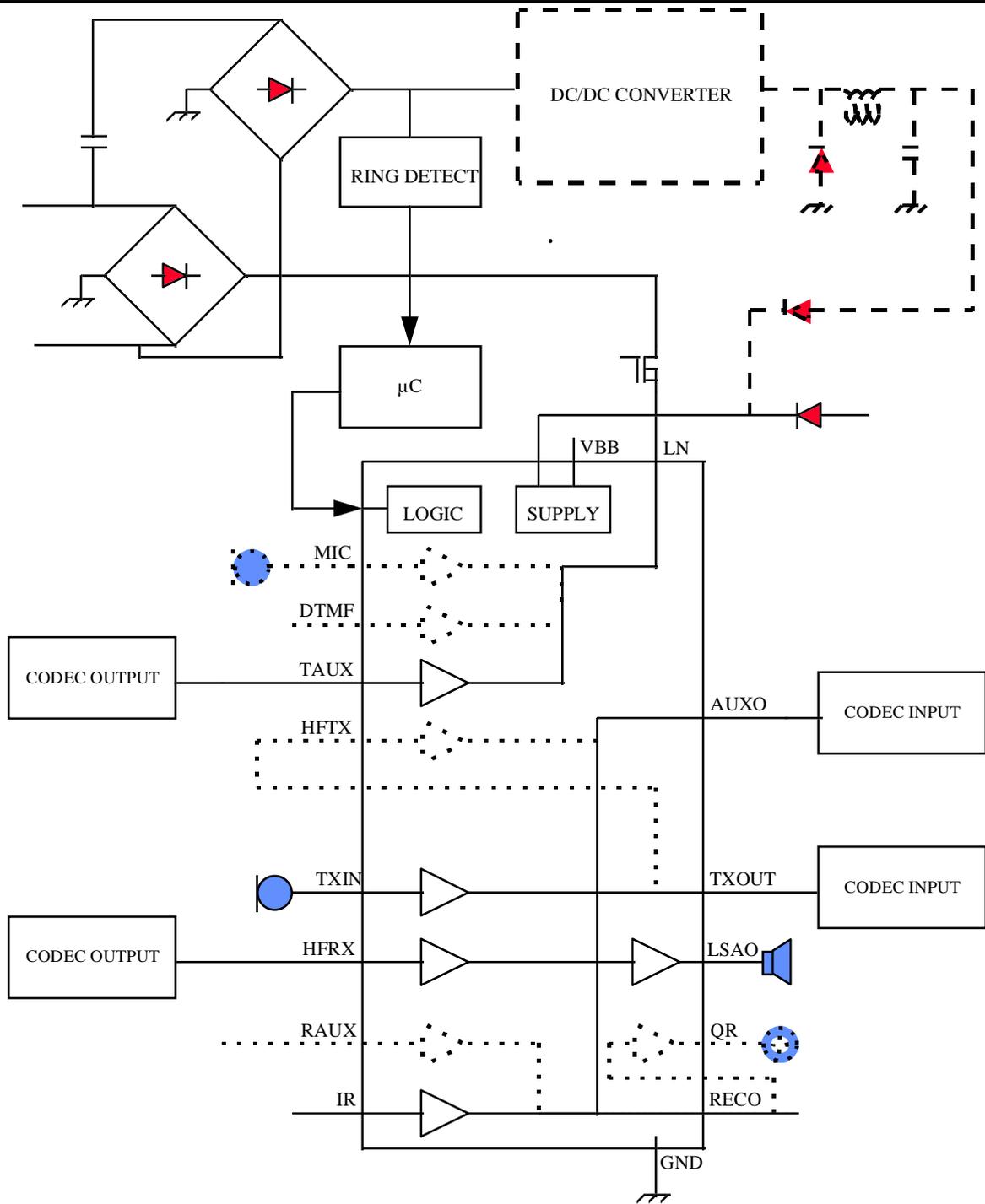


Fig. 50 Digital Handsfree application

TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer

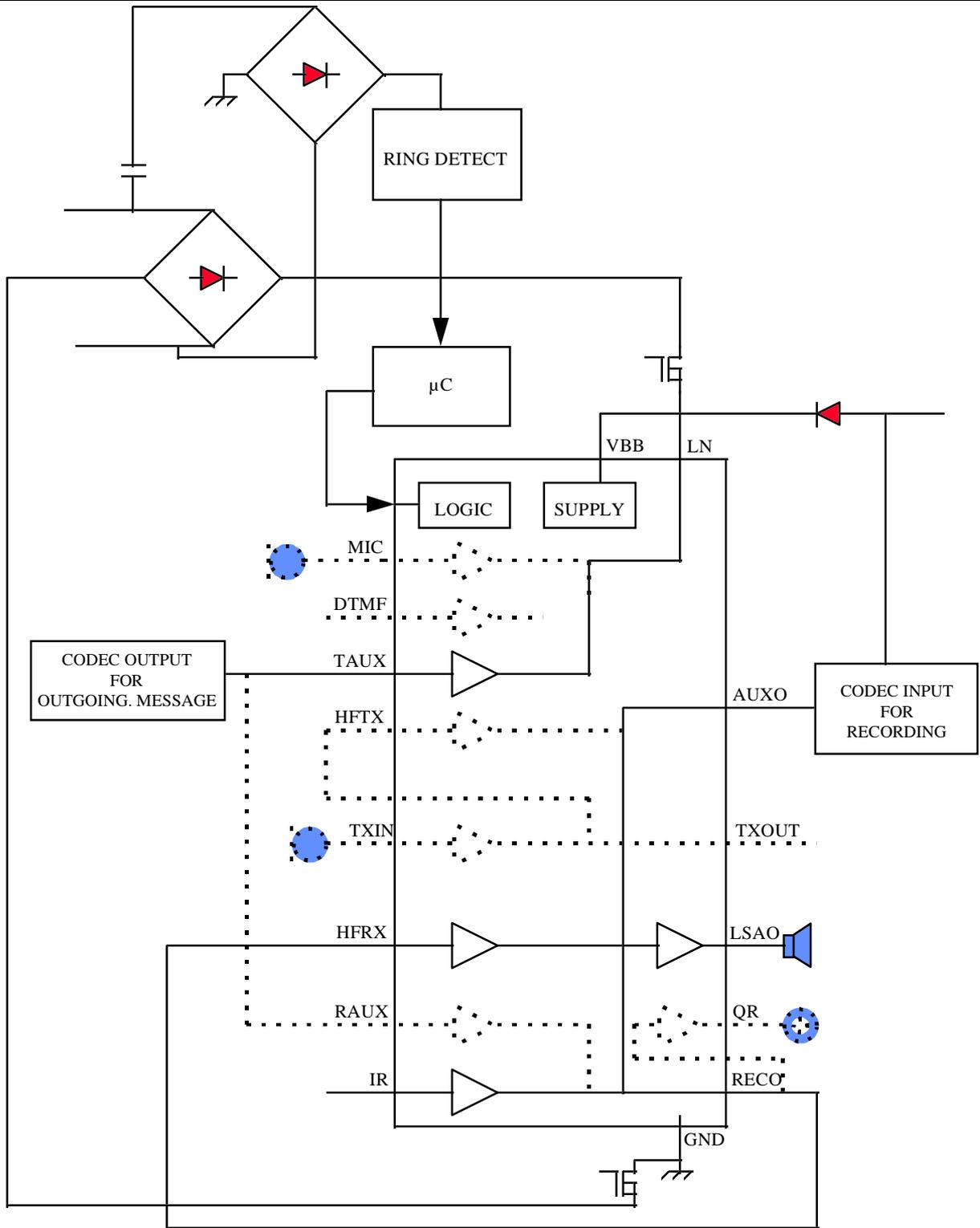


Fig. 51 Answering Machine "on line"

TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer

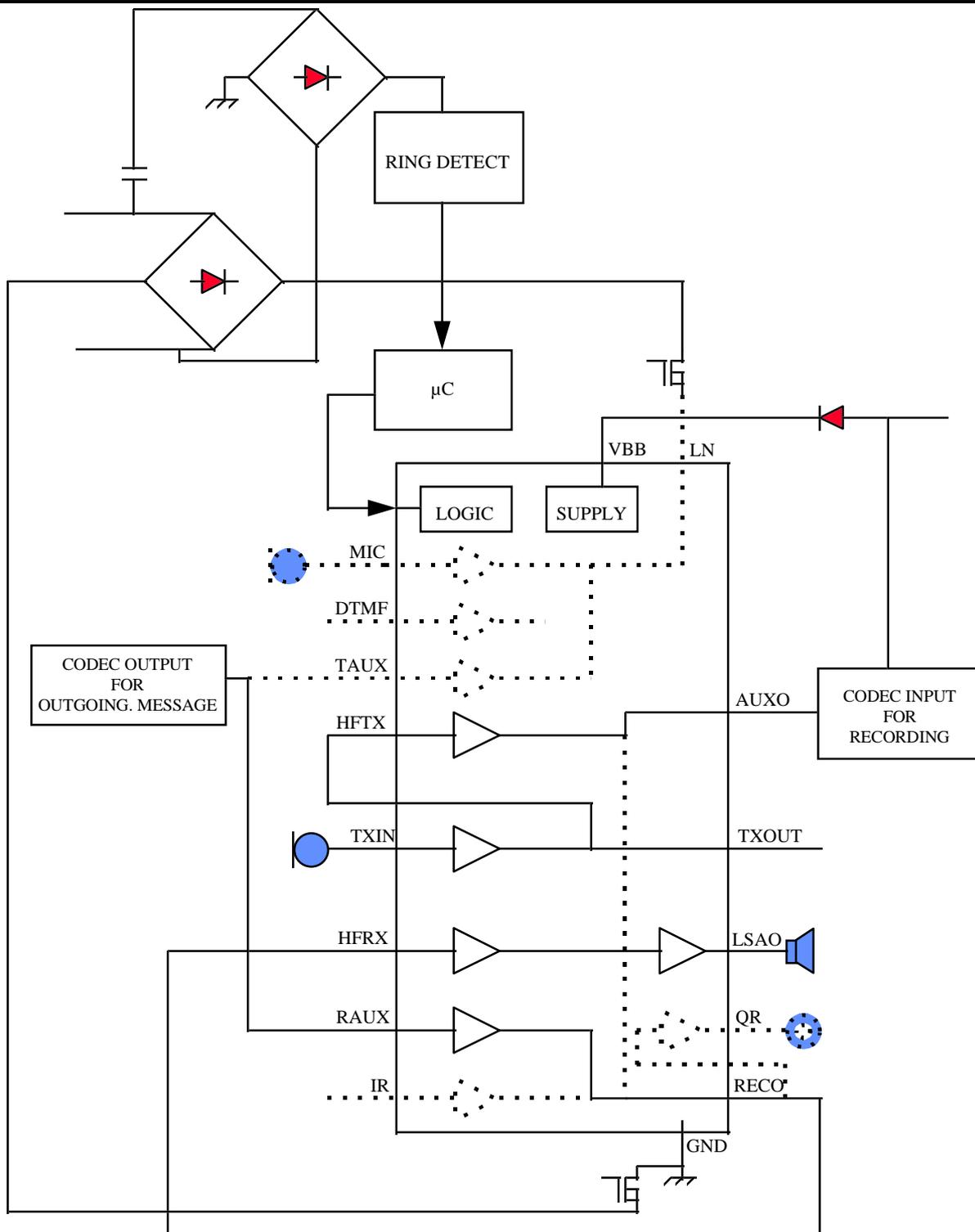


Fig. 52 Answering Machine: record, listen with base

TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer

Application Note

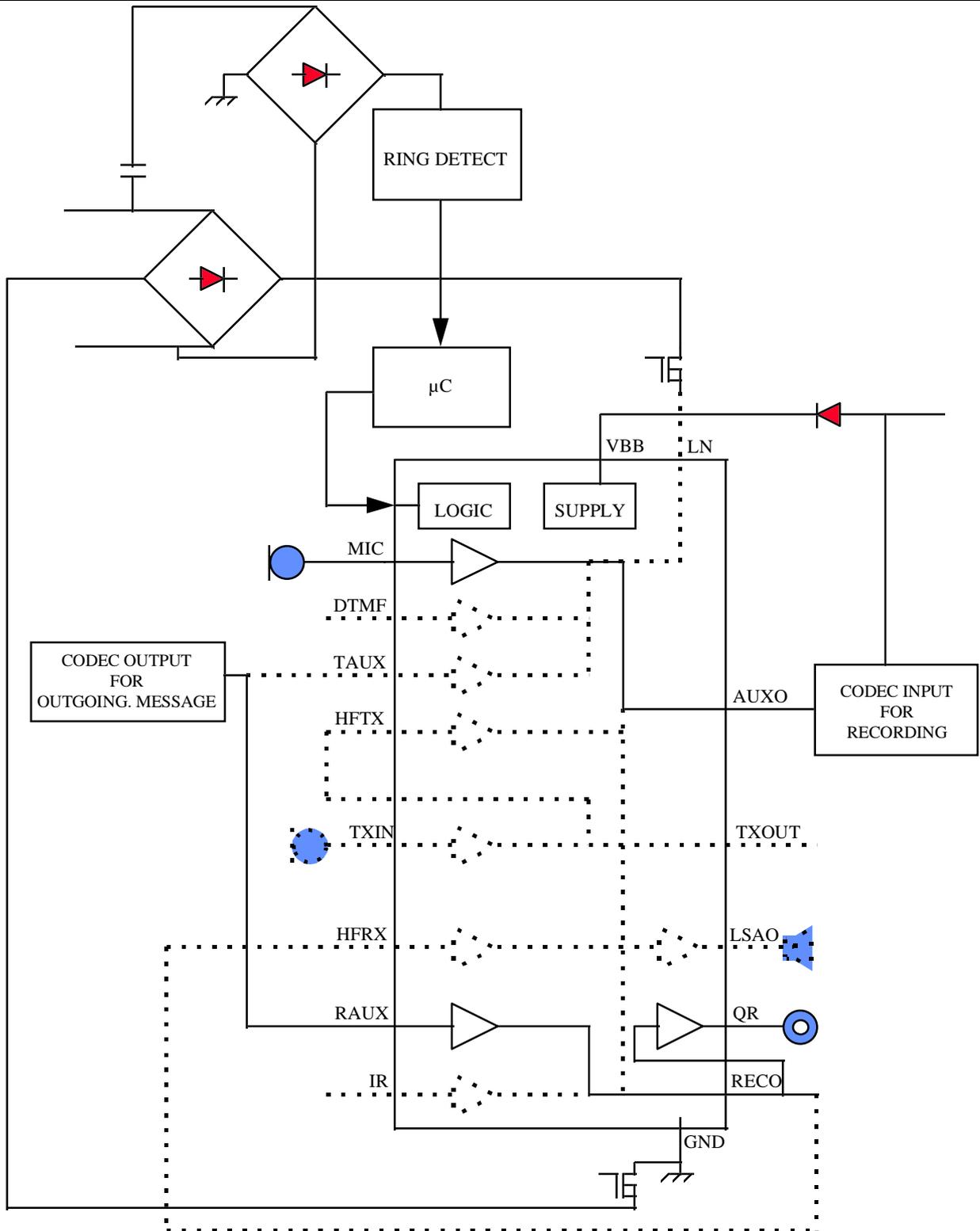


Fig. 53 Answering Machine: record or listen with handset

TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer

Application Note

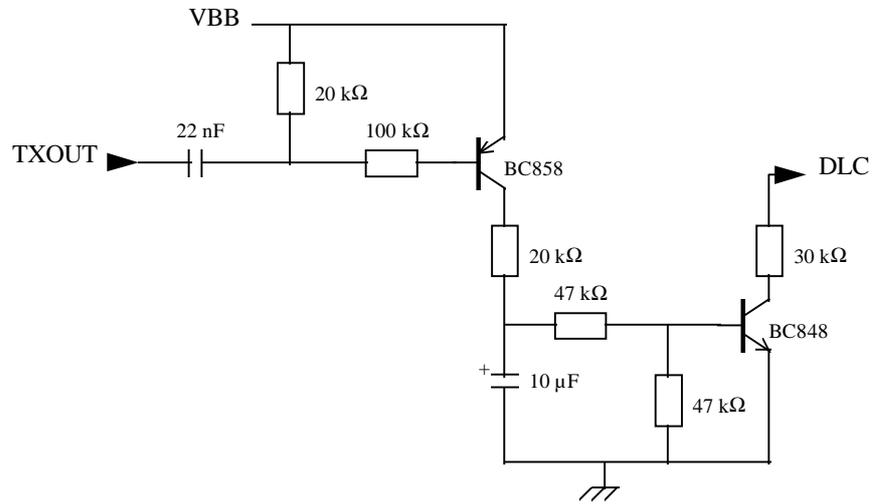


Fig. 54 Typical external antihowling circuit

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

6. ELECTROMAGNETIC COMPATIBILITY

As no common international specification exists for RFI immunity, and as different assembly methods may lead to different solutions, only some advices can be provided.

It is advisable to take care of the impedance of the GND, the smallest is always the best. Even if it is required to separate low level microphone signals on GNCTX from high level signals (loudspeaker or others), GND and GNCTX traces must be as wide as possible.

Also, the connection of Rstab, Rgatz, Rgals and Re2 has to be done with very short traces (specially STAB input which sets all the gains must be very immune).

VOL, MIC+/MIC-, HFTX, TXAUX and TXIN inputs may also be sensitive (RF signals entering these pins would be amplified). Rvol must preferably be connected with short traces or VOL input may be lightly decoupled by a capacitor to GND or better the trace must be inserted between GND traces. Care has to be taken with the layout of the microphone amplifiers, which is also helpful for the noise, providing a good decoupling to GNCTX. Low-pass RC filters may be added at the inputs of the amplifiers (C3, C4, C8 on the demoboard). The output TXOUT may also be sensitive to high interference, it can be decoupled to GNCTX with a small capacitor (<56pF, Ctxor on the demoboard).

It can be helpful to decouple the receive input IR, two possibilities are offered: a capacitor smaller than 220 pF between IR and GND (C10 on the demoboard) or a capacitor lower than 2.2 nF between IR and LN (C21 on the demoboard).

It is not allowed to put a capacitor directly between STAB and GND, only an RC network could be implemented if it helps (365 Ω , 4.7 nF).

Low impedance capacitors in parallel with the electrolytic one between VBB and GND may help.

Usually a low impedance capacitor connected between LN and GND helps for the conducted interferences, but this capacitor is in parallel with the impedance network of the apparatus, so, its value must be small enough.

In general when connections are coming from external environment (e.g. MIC+, MIC-, A, B on the demoboard), it is better to filter the RFI signal before it influences the close environment of the TEA1097 (e.g. action of C1,C2, C6, C11 which are close to the connectors on the demoboard).

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

7. REFERENCES

- [1] **TEA1097** Speech and Handsfree IC with auxiliary inputs/output and analog multiplexer
Device specification

- [2] OM5848 Speech and Handsfree IC with auxiliary inputs/output and analog multiplexer Demonstration board
User Manual

- [3] Philips Semiconductors
SEMICONDUCTORS FOR WIRED TELECOM SYSTEMS - IC03a -
Data handbook

- [4] Philips Semiconductors
SEMICONDUCTORS FOR WIRED TELECOM SYSTEMS - IC03b -
Application handbook

- [5] PCD6002 Digital telephone answering machine chip
Device specification

**TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer**

Application Note**APPENDIX****LIST OF ABBREVIATIONS AND DEFINITIONS**

AGC	Automatic line loss compensation of the TEA1097
A.M.	Answering machine
Ast	Sidetone gain
AUXC	Logic input
AUXO	Auxiliary amplifier output of TEA1097
BRL	Balance Return Loss: matching between the apparatus impedance and a reference
Cgar	Capacitor setting receive path amplifier low-pass filter
Catx	Capacitor setting the base microphone amplifier low-pass filter
Cfeed	Microphone supply filter capacitor
Chrx	Receive input capacitor
Chfx	Transmit output capacitor
Clso	Loudspeaker coupling capacitor
Cmicb/h	Microphone low-pass filter capacitors
Ctxin	Base microphone amplifier input capacitor
dBmp	dBm psophometrically weighted (0dBmp=1mW)
dBVp	dBV psophometrically weighted (0dBVp=1Vrms)
DTMF	Dual Tone Multi Frequency
GALS	Loudspeaker amplifier gain adjustment pin
GARX	Earphone amplifier gain adjustment pin
GATX	Base microphone gain adjustment pin
GL	Group-listening
GND	Ground reference pin
GNDTX	Ground reference pin for microphone signals
HF	Handsfree
HFC	Logic input
HFRX	Loudspeaker amplifier receive input
HFTX	Base microphone auxiliary input
IR	Receive input from line
Istart	Start current of the AGC function

**TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer**

Application Note

Istop	Stop current of the AGC function
k	Scale factor of anti-sidetone network
Leq	Artificial inductor of the voltage stabilizer
LN	Positive line terminal of TEA1097
LSAO	Loudspeaker amplifier output of TEA1097
MIC+,MIC-	Microphone input of TEA1097
MICS	Microphone supply of TEA1097
MOSFET	Meta Oxide Field Effect Transistor
MUTT/	Logic input
MUTR/	Logic input
PCB	Printed circuit board
PD/	Logic input (power-down input)
PTAT	Proportional to absolute temperature
PTT	Public telephone company
QR	Earphone amplifier output of TEA1097
RAUX	Auxiliary receive input
RECO	Receive output from line
REG	Filter capacitor of the equivalent inductor connection pin of the TEA1097
Rexch	Bridge resistance of exchange
RFI	Radio frequency interference
Rgatx	Resistor setting base microphone amplifier gain
Rload	Loudspeaker equivalent load resistor
Rmicm/p	Resistors setting microphone sensitivities
Rp	Internal resistance between LN and REG
Rslpe	Resistor setting slope of the DC characteristic of TEA1097
Rstab	Resistor setting an internally used PTAT current
Rva	Voltage adjustment resistor
Rvol	Volume control potentiometer
SLPE	DC slope pin of TEA1097
STAB	Reference current pin
THD	Total Harmonic Distortion (%)
TXAUX	Auxiliary transmit input
TXIN	Base microphone amplifier input
TXOUT	Base microphone amplifier output

**TEA1097 Speech and loudspeaker amplifier IC
with auxiliary inputs/outputs and analog multiplexer**

Application Note

VBB	Positive supply of TEA1097
VDD	Microcontroller supply of TEA1097
VIn	DC voltage between LN and GND
VOL	Volume adjustment pin
Vref	Stabilized reference voltage between LN and SLPE
Vslpe	DC voltage level between SLPE and LN
Zir	Input impedance of the receive amplifier of the TEA1097
Zbal	Anti-sidetone network
α	Gain control factor of the AGC

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

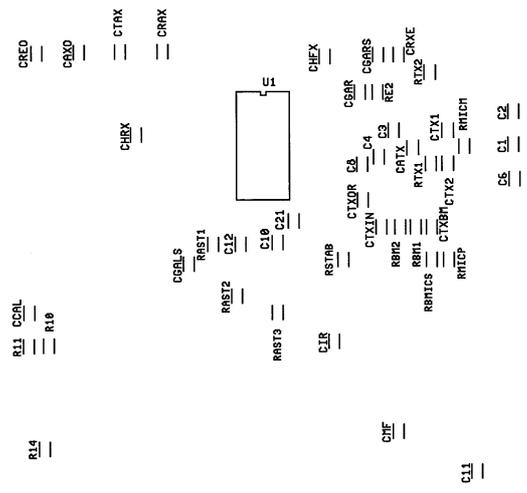
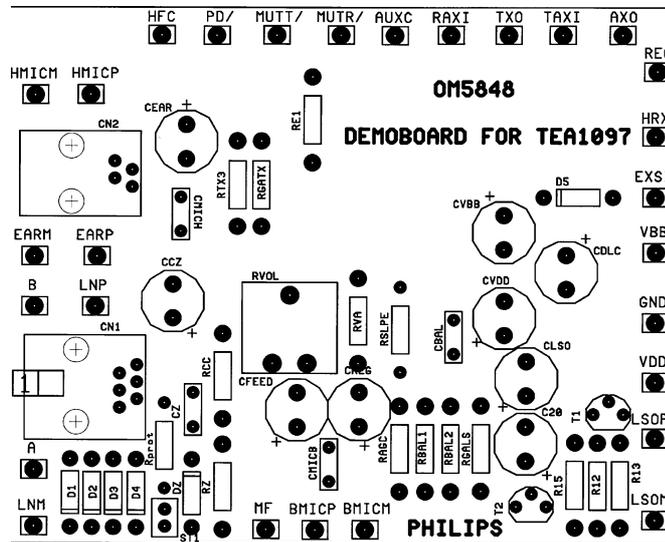


Fig. 56 component placement diagram of the demoboard

TEA1097 Speech and loudspeaker amplifier IC with auxiliary inputs/outputs and analog multiplexer

Application Note

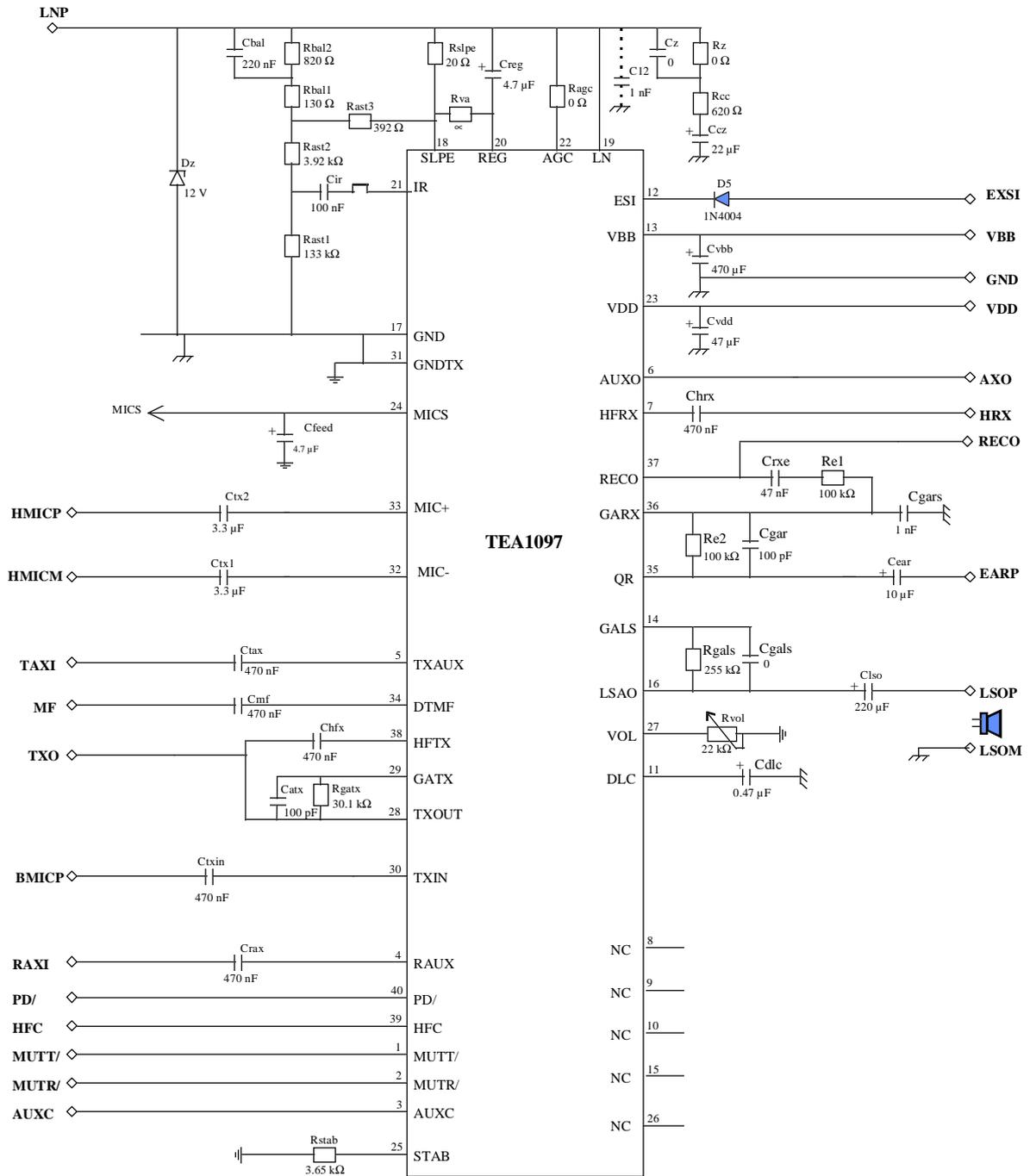


Fig. 57 Curve ref board of the TEA1097